

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17MAT31

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Engineering Mathematics – III

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing
ONE full question from each module.**

Module-1

- 1 a. Find the Fourier series expansion for the periodic function $f(x)$, if in one second
- $$f(x) = \begin{cases} 0; & -\pi < x < 0 \\ x; & 0 < x < \pi \end{cases} \quad (08 \text{ Marks})$$
- b. Expand the function $f(x) = x(\pi-x)$ over the interval $(0, \pi)$ in half range Fourier cosine series. (06 Marks)
- c. The following value of function y gives the displacement in inches of a certain machine part for rotations x of a flywheel. Expand y -in terms of Fourier series upto the second harmonic.

Rotations	x	0	$\pi/6$	$2\pi/6$	$3\pi/6$	$4\pi/6$	$5\pi/6$	π
Displacement	y	0	9.2	14.4	17.8	17.3	11.7	0

(06 Marks)

OR

- 2 a. Find the Fourier series expansion for the function :
- $$f(x) = \begin{cases} \pi x; & 0 \leq x \leq 1 \\ \pi(2-x); & 1 \leq x \leq 2 \end{cases}$$
- and deduce $\frac{\pi^2}{8} = \sum_{n=1}^{\infty} \frac{1}{(2n-1)^2}$. (08 Marks)
- b. Expand in Fourier series $f(x) = (\pi-x)^2$ over the interval $0 \leq x \leq 2\pi$. (06 Marks)
- c. The following table gives the variations of periodic current over a period T .

t (secs)	0	$T/6$	$T/3$	$T/2$	$2T/3$	$5T/6$	T
A (Amps)	1.98	1.30	1.05	1.30	-0.88	-0.25	1.98

Expand the function (periodic current) by Fourier series and show that there is a direct current part of 0.75 amp and also obtain amplitude of first harmonic. (06 Marks)

Module-2

- 3 a. Find Fourier transform of $f(x) = \begin{cases} 1-x^2; & |x| < 1 \\ 0; & |x| > 1 \end{cases}$
- and hence evaluate $\int_0^{\infty} \frac{x \cos x - \sin x}{x^3} dx$. (08 Marks)
- b. Find Fourier Cosine transform of the function :
- $$f(x) = \begin{cases} 4x; & 0 < x < 1 \\ 4-x; & 1 < x < 4 \\ 0; & x > 4 \end{cases} \quad (06 \text{ Marks})$$
- c. Find z-transforms of: i) $a^n \sin n\theta$ ii) $a^{-n} \cos n\theta$. (06 Marks)

OR

- 4 a. Find Fourier sine transform of $f(x) = e^{-|x|}$ and hence evaluate : $\int_0^{\infty} \frac{x \sin mx}{1+x^2} dx, m > 0$. (08 Marks)
- b. Find z-transform of $u_n = \cos h\left(\frac{n\pi}{2} + 0\right)$. (06 Marks)
- c. Solve the difference equation using z-transforms $u_{n+2} + 6u_{n+1} + 9u_n = 2^n$. Given $u_0 = u_1 = 0$. (06 Marks)

Module-3

- 5 a. If θ - is the acute angle between the two regression lines relating the variables x and y , show that $\text{Tan}\theta = \left(\frac{1-r^2}{r}\right) \left(\frac{\sigma_x \sigma_y}{\sigma_x^2 \sigma_y^2}\right)$. (08 Marks)
- Indicate the significance of the cases $r = \pm 1$ and $r = 0$.
- b. Fit a straight line $y = ax + b$ for the data.

x	12	15	21	25
y	50	70	100	120

- (06 Marks)
- c. Find a real root of the equation by using Newton-Raphson method near $x = 0.5$, $xe^x = 2$, perform three iterations. (06 Marks)

OR

- 6 a. Compute the coefficient of correlation and equation of regression of lines for the data :

x	1	2	3	4	5	6	7
y	9	8	10	12	11	13	14

(08 Marks)

- b. The Growth of an organism after x - hours is given in the following table :

x (hours)	5	15	20	30	35	40
y (Growth)	10	14	25	40	50	62

- Find the best values of a and b in the formula $y = ae^{bx}$ to fit this data. (06 Marks)
- c. Find a real root of the equation $\cos x = 3x - 1$ correct to three decimals by using Regula - False position method, given that root lies in between 0.6 and 0.7. Perform three iterations. (06 Marks)

Module-4

- 7 a. Find $y(8)$ from $y(1) = 24$, $y(3) = 120$, $y(5) = 336$, $y(7) = 720$ by using Newton's backward difference interpolation formula. (08 Marks)
- b. Define $f(x)$ - as a polynomial in x for the following data using Newton's divided difference formula. (06 Marks)

x	-4	-1	0	2	5
f(x)	1245	33	5	9	1335

- c. Evaluate the integral $I = \int_0^6 \frac{dx}{4x+5}$ using Simpson's $\frac{1}{3}$ rd rule using 7 ordinates. (06 Marks)

OR

- 8 a. For the following data calculate the differences and obtain backward difference interpolation polynomial. Hence find $f(0.35)$. (08 Marks)

x	0.1	0.2	0.3	0.4	0.5
f(x)	1.40	1.56	1.76	2.0	2.28

- b. Using Lagrange's interpolation find y when $x = 10$.

x	5	6	9	11
y	12	13	14	16

- c. Evaluate $\int_0^1 \frac{x}{1+x^2} dx$ by Weddle's rule considering seven ordinates. (06 Marks)

Module-5

- 9 a. Verify the Green's theorem in the plane for $\int_C (x^2 + y^2)dx + 3x^2y dy$ where C – is the circle $x^2 + y^2 = 4$ traced in positive sense. (08 Marks)
- b. Evaluate $\int_C (\sin z dx - \cos x dy + \sin y dz)$ by using Stokes theorem, where C – is the boundary of the rectangle $0 \leq x \leq \pi$, $0 \leq y \leq 1$ and $z = 3$. (06 Marks)
- c. Find the curve on which the functional: $\int_0^1 [y'^2 + 12xy]dx$ with $y(0) = 0$, $y(1) = 1$ can be extremised. (06 Marks)

OR

- 10 a. Given $f = (3x^2 - y)i + xzj + (yz - x)k$ evaluate $\int_C f \cdot dr$ from $(0, 0, 0)$ to $(1, 1, 1)$ along the paths $x = t$, $y = t^2$ and $z = t^3$. (08 Marks)
- b. Derive Euler's equation in the form $\frac{\partial f}{\partial y} - \frac{d}{dx} \left(\frac{\partial f}{\partial y'} \right) = 0$. (06 Marks)
- c. Prove that the shortest distance between two points in a plane is a straight line. (06 Marks)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--

17MATDIP31

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Additional Mathematics - I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Prove that $(1 + \cos\theta + i \sin\theta)^n + (1 + \cos\theta - i \sin\theta)^n = 2^{n+1} \cos^n\left(\frac{\theta}{2}\right) \cos\left(\frac{n\theta}{2}\right)$ (08 Marks)
- b. Express $\sqrt{3} + i$ in the polar form and hence find its modulus and amplitude. (06 Marks)
- c. Find the sine of the angle between vectors $\vec{a} = \hat{i} + \hat{j} + \hat{k}$ and $\vec{b} = 2\hat{i} - 3\hat{j} + 2\hat{k}$ (06 Marks)

OR

- 2 a. Express $\frac{3 + 4i}{3 - 4i}$ in the form $x + iy$. (08 Marks)
- b. If the vector $2\hat{i} + \lambda\hat{j} + \hat{k} = 0$ and $4\hat{i} - 2\hat{j} - 2\hat{k}$ are perpendicular to each other, find λ . (06 Marks)
- c. Find λ , such that the vectors $2\hat{i} - \hat{j} + \hat{k}$, $\hat{i} + 2\hat{j} - 3\hat{k}$, $3\hat{i} + \lambda\hat{j} + 5\hat{k}$ are coplanar. (06 Marks)

Module-2

- 3 a. If $y = e^{a \sin^{-1} x}$, prove that $(1 - x^2)y_{n+2} - (2n + 1)xy_{n+1} - (n^2 + a^2)y_n = 0$ (08 Marks)
- b. With usual notations, prove that $\tan\phi = r \frac{d\theta}{dr}$. (06 Marks)
- c. If $u = \log_e \frac{x^3 + y^3}{x^2 + y^2}$, prove that $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = 1$. (06 Marks)

OR

- 4 a. Using Maclaurin's series, expand $\tan x$ upto the term containing x^5 . (08 Marks)
- b. Find the pedal equation of $r = a(1 - \cos\theta)$. (06 Marks)
- c. If $u = x + 3y^2 - z^3$, $v = 4x^2yz$ and $w = 2z^2 - xy$, find $\frac{\partial(u, v, w)}{\partial(x, y, z)}$ at $(1, -1, 0)$. (06 Marks)

Module-3

- 5 a. Obtain a reduction formula for $\int_0^{\pi/2} \cos^n x \, dx$, ($n > 0$). (08 Marks)
- b. Evaluate $\int_0^a \frac{x^7}{\sqrt{a^2 - x^2}} \, dx$ (06 Marks)
- c. Evaluate $\int_1^2 \int_1^3 xy^2 \, dx \, dy$ (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Obtain a reduction formula for $\int_0^{\pi/2} \sin^n x \, dx$, ($n > 0$). (08 Marks)
- b. Evaluate $\int_0^{2a} x^2 \sqrt{2ax - x^2} \, dx$ (06 Marks)
- c. Evaluate $\int_{-1}^1 \int_0^z \int_{x-z}^{x+z} (x + y + z) \, dx \, dy \, dz$ (06 Marks)

Module-4

- 7 a. A particle moves along the curve $x = 2t^2$, $y = t^2 - 4t$ and $z = 3t - 5$, where 't' is the time. Find its velocity and acceleration vectors and also magnitude of velocity and acceleration at $t = 1$. (08 Marks)
- b. In which direction of the directional derivative of x^2yz^3 is maximum at $(2, 1, -1)$ and find the magnitude of this maximum. (06 Marks)
- c. Show that $\vec{F} = (y + z)\hat{i} + (x + z)\hat{j} + (x + y)\hat{k}$ is irrotational. (06 Marks)

OR

- 8 a. If $\phi = xy^2z^3 - x^3y^2z$, find $\nabla\phi$ and $|\nabla\phi|$ at $(1, -1, 1)$. (08 Marks)
- b. If $\vec{F} = (x + y + 1)\hat{i} + \hat{j} - (x + y)\hat{k}$, show that $\vec{F} \cdot \text{Curl}\vec{F} = 0$. (06 Marks)
- c. If $x = t^2 + 1$, $y = 4t - 3$, $z = 2t^2 - 6t$ represents the parametric equation of a curve, find the angle between the tangents at $t = 1$ and $t = 2$. (06 Marks)

Module-5

- 9 a. Solve: $\left(x \tan \frac{y}{x} - \frac{y}{x} \sec^2 \frac{y}{x} \right) dx = x \sec^2 \frac{y}{x} dy$ (08 Marks)
- b. Solve: $xy(1 + xy^2) \frac{dy}{dx} = 1$ (06 Marks)
- c. Solve: $\frac{dy}{dx} + \frac{y \cos x + \sin y + y}{\sin x + x \cos y + x} = 0$ (06 Marks)

OR

- 10 a. Solve: $(3y + 2x + 4)dx - (4x + 6y + 5)dy = 0$ (08 Marks)
- b. Solve: $(1 + y^2)dx = (\tan^{-1}y - x)dy$ (06 Marks)
- c. Solve: $(y \log y)dx + (x - \log y)dy = 0$. (06 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC32

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing
ONE full question from each module.**

Module-1

- 1 a. Define the following terms:
 - i) Accuracy and precision
 - ii) Grass error and systematic error. (06 Marks)
- b. Draw the block diagram of a true RMS volt meter and explain its operation. (07 Marks)
- c. Calculate series connected multiplier resistance with a D'Arsonval movement with an internal resistance of 50Ω and full scale deflection current of 2mA in to a multi range d.c. voltmeter with range from 0 – 10V, 0 – 50V, 0 – 100V and 0 – 250V. (07 Marks)

OR

- 2 a. State different types of thermocouple used for RF current measurement and explain each one of them in brief. (07 Marks)
- b. Sketch and explain the operation of a Multirange Ammeter and Ayrton shunt. (07 Marks)
- c. The expected value of the voltage across a resistor is 75V, But measurement gives a value of 74V, calculate:
 - i) Absolute error
 - ii) % error
 - iii) Relative accuracy and
 - iv) % of accuracy. (06 Marks)

Module-2

- 3 a. Describe with a diagram the operation of a successive approximation type DVM. (07 Marks)
- b. Explain with a diagram the working of digital pH meter. (07 Marks)
- c. A $4\frac{1}{2}$ digits DVM is used for voltage measurements. Find:
 - i) Resolution
 - ii) How would 67.50V be displayed on 5V range
 - iii) How would 0.716V be displayed on 10V range. (06 Marks)

OR

- 4 a. Describe with the help of a diagram the operation of universal counter. (07 Marks)
- b. Explain with block diagram digital phase meter operation. (06 Marks)
- c. With the block diagram, explain the digital frequency meter. (07 Marks)

Module-3

- 5 a. Draw the basic block diagram of an oscilloscope and explain the function of each block. (08 Marks)
- b. Sketch the block diagram and explain AF Sine and square wave generator. (07 Marks)
- c. Discuss the important features of Cathode Ray Tube (CRT). (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. With block diagram, explain the working of DSO and list the advantages of it. (08 Marks)
b. Explain the function generator with suitable diagram. (07 Marks)
c. Discuss frequency measurement with Lissajous figure. (05 Marks)

Module-4

- 7 a. With circuit diagram, explain Q-meter and mention its application. (06 Marks)
b. Draw the circuit of a Wheatstone's bridge and explain how it can be used to measure unknown resistance. (06 Marks)
c. Draw the circuit diagram and obtain the balance condition for Maxwell's bridge. If bridge contents are $C_1 = 0.5 \mu\text{F}$, $R_1 = 1200\Omega$, $R_2 = 700\Omega$ and $R_3 = 300\Omega$ find resistance and inductance of the coil. (08 Marks)

OR

- 8 a. What is Meggar? Explain the basic Meggar circuit. (08 Marks)
b. With neat diagram, explain the working of Wien's bridge? How it can be used as oscillator. (08 Marks)
c. A capacitance comparison bridge is used to measure a capacitive impedance at a frequency of 2kHz the bridge constants at balance are $C_3 = 100\mu\text{F}$, $R_1 = 10\text{K}\Omega$, $R_2 = 50\text{K}\Omega$ and $R_3 = 100\text{K}\Omega$. Find the equivalent series circuit of the unknown impedance. (04 Marks)

Module-5

- 9 a. List the factors to be considered while selecting transducers. (06 Marks)
b. Explain principle operation of resistive position transducer. (06 Marks)
c. Derive an expression for gauge factor for Bonded resistance wire strain gauges. (08 Marks)

OR

- 10 a. Explain the construction and operation of LVDT show the characteristic curve. (08 Marks)
b. Explain Piezoelectric transducer. (06 Marks)
c. Explain semiconductor photo diode and photo transistor. (06 Marks)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC33

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Analog Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Derive an expression for input impedance, output impedance, voltage gain and current gain of un bypassed RE common emitter amplifier using r_e model. (10 Marks)
- b. For the network of Fig.Q1(b), determine : i) r_e ii) Z_i iii) Z_o , ($r_0 = \infty\Omega$) iv) $A_v(r_0 = \infty\Omega)$ v) the parameters of parts ii through iv if $r_0 = 50K\Omega$ for $R_1 = 56K\Omega$, $R_2 = 8.2K\Omega$, $C_1 = 10\mu f$, $C_2 = 10\mu f$, $R_E = 1.5K\Omega$, $C_E = 20\mu f$, $R_C = 6.8K\Omega$, $\beta = 90$ and $V_{CC} = 22V$. (10 Marks)

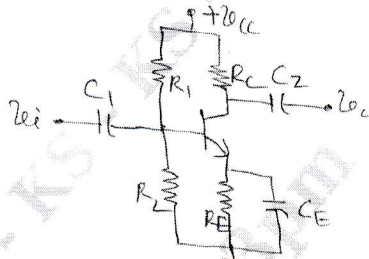


Fig.Q1(b)

OR

- 2 a. Derive an expression of input impedance, output impedance, voltage gain and current gain of fixed bias CE amplifier using h-parameter. (10 Marks)
- b. Determine r_e , h_{fe} , h_{ie} , Z_i , Z_o , A_v and A_i for the circuit shown in Fig.Q2(b) using hybrid equivalent model. (10 Marks)

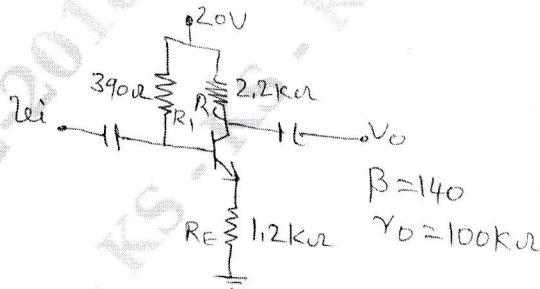


Fig.Q2(b)

Module-2

- 3 a. Explain the working principle of JFET, and explain the transfer characteristics of JFET. (08 Marks)
- b. Derive an expression for input impedance, output impedance, voltage gain and current gain of fixed bias FET amplifier. (08 Marks)
- c. Distinguish between JFET and MOSFET. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 4 a. With neat diagram explain construction and working principle of n-channel depletion type MOSFET. (10 Marks)
- b. Derive an expression for input impedance, output impedance and voltage gain of common – Gate FET amplifier. (10 Marks)

Module-3

- 5 a. Derive an expression for low frequency response of BJT amplifier due to capacitors C_S , C_E and C_C . (10 Marks)
- b. Determine the lower cutoff frequency for the network of Fig.Q5(b) using the following parameters $C_i = 10\mu\text{f}$, $C_E = 20\mu\text{f}$, $C_C = 1\mu\text{f}$, $R_S = 1\text{k}\Omega$, $R_1 = 40\text{K}\Omega$, $R_2 = 10\text{K}\Omega$, $R_E = 2\text{K}\Omega$, $R_C = 4\text{K}\Omega$, $R_L = 2.2\text{K}\Omega$, $\beta = 100$, $r_o = \infty\Omega$ and $V_{CC} = 20\text{V}$, plot the response. (10 Marks)

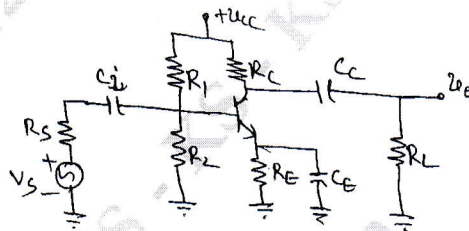


Fig.Q5(b)

OR

- 6 a. Define Miller's theorem, determine equivalent input and output capacitances of the circuit. (10 Marks)
- b. Determine the lower cutoff frequency for the network of Fig.Q6(b) using the following parameters. $C_G = 0.01\mu\text{f}$, $C_C = 0.5\mu\text{f}$, $C_S = 2\mu\text{f}$, $R_{\text{sig}} = 10\text{K}\Omega$, $R_G = 1\text{M}\Omega$, $R_0 = 4.7\text{K}\Omega$, $R_S = 1\text{K}\Omega$, $R_L = 2.2\text{K}\Omega$, $I_{DSS} = 8\text{mA}$, $V_P = -4\text{V}$, $r_d = \infty\Omega$, $V_{DD} = 20\text{V}$, $V_{GSQ} = -2\text{V}$ and $I_{DQ} = 2\text{mA}$. Plot the frequency response. (10 Marks)

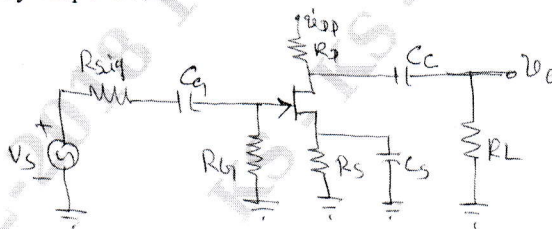


Fig.Q6(b)

Module-4

- 7 a. Determine input resistance and output resistance of voltage shunt feedback amplifier. (06 Marks)
- b. Determine the voltage, input and output impedance with feedback for voltage series feedback having $A = 100$, $R_i = 10\text{K}\Omega$ and $R_o = 20\text{K}\Omega$ for feedback of i) $\beta = 0.1$ ii) $\beta = 0.5$. (07 Marks)
- c. Explain the characteristics of negative feedback amplifier. (07 Marks)

OR

- 8 a. What is Barkhausen criteria for sustained oscillation? Explain basic principle of operation of oscillators. (08 Marks)
- b. Explain the working of Wein bridge oscillator. Write the equation for frequency of oscillations. (08 Marks)
- c. For the colpitts oscillators, $C_1 = 0.005\mu\text{f}$, $C_2 = 0.01\mu\text{f}$, $L = 100\mu\text{H}$, $L_{\text{PFC}} = 0.5\text{mH}$, $C_C = 10\mu\text{f}$ and $h_{fe} = 110$.
- Calculate frequency of oscillation
 - Check the condition for oscillation is satisfied. (04 Marks)

Module-5

- 9 a. Explain the operation of transformer coupled class – A power amplifier and show that the maximum percentage efficiency is 50%. (07 Marks)
- b. Explain with neat circuit diagram, the working of a complementary symmetry class – B amplifier. (07 Marks)
- c. Derive an expression for second harmonic distortion using 3 – point method. (06 Marks)

OR

- 10 a. Define voltage regulator. Explain the operation of series regulator circuit. (07 Marks)
- b. Explain the operation of shunt regulator using OP-Amp with neat circuit diagram. (07 Marks)
- c. Calculate the output voltage and Zener current in the regulator circuit of Fig.Q10(c) for $R_L = 1\text{K}\Omega$, $V_z = 12\text{V}$, $R = 220\Omega$, $v_i = 20\text{V}$ and $\beta = 50$. (06 Marks)

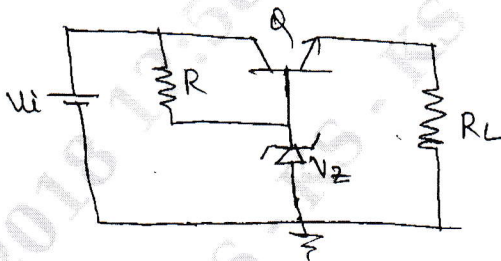


Fig.Q10(c)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC34

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Convert $x = \bar{a}b + bc$ to canonical SOP form. (02 Marks)
- b. Simplify $G = f(w, x, y, z) = \pi M(1,3,8,10,12,13,14,15)$ in POS form and implement using NOR gates. (08 Marks)
- c. Simplify the following using Quine-McClusky's minimization technique.
 $V = f(a, b, c, d) = \sum m(1, 3, 4, 5, 6, 9, 11, 12, 13, 14)$ (10 Marks)

OR

- 2 a. Convert $P = (\bar{w} + x)(y + \bar{z})$ to canonical POS form. (03 Marks)
- b. Simplify $P = f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$ in SOP form and implement using NAND gates. (07 Marks)
- c. Simplify using Quine-McClusky's minimization technique:
 $V = f(a, b, c, d) = \sum m(1, 5, 7, 9, 13, 15) + \sum d(8, 10, 11, 14)$ (10 Marks)

Module-2

- 3 a. Implement $f_1(a, b, c) = \sum m(1, 3, 5)$; $f_2(a, b, c) = \sum m(0, 1, 6)$ using 74138, 3:8 decoder. (06 Marks)
- b. With a neat circuit diagram explain the carry look ahead adder with relevant expressions. (10 Marks)
- c. Design a one-bit comparator, implement using suitable gates. (04 Marks)

OR

- 4 a. Using 74151, 8:1 Mux, realize the Boolean function $F(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 10, 15)$ with b, c, d as select lines. (04 Marks)
- b. With neat circuit diagram, explain the keypad interface using 74147, 10 line to BCD encoder. (10 Marks)
- c. Design a full subtractor and implement using logic gates. (06 Marks)

Module-3

- 5 a. Discuss the working principle of Gated SR latch with its truth Table. (06 Marks)
- b. Explain the operation of Switch debouncer built using SR latch with the help of circuit and waveforms. (08 Marks)
- c. Obtain the characteristic equations of JK flip flop and SR flip flop. (06 Marks)

OR

- 6 a. What is race around condition? How it can be overcome? (02 Marks)
- b. Explain the working of MS-JK flip flop with logic symbol and timing diagram. (10 Marks)
- c. Explain the working of +ve edge triggered D flip flop with the functional table. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. Explain the working of four bit ripple counter using +ve edge triggered T flip-flops with the counting sequence table and timing diagram. (10 Marks)
 b. Explain the SIPO and SISO operation of shift register with relevant logic diagram and the truth table. (06 Marks)
 c. Explain the operation of ring counter using logic diagram and truth table. (04 Marks)

OR

- 8 a. Explain Universal Shift Register with the help of logic diagram and mode control table. (10 Marks)
 b. Realize a three-bit binary synchronous up counter using JK flip flops. (10 Marks)

Module-5

- 9 a. Construct a Mealy state diagram that will detect input sequence 10110, when input pattern is detected Z is asserted high. Write the state diagram. (10 Marks)
 b. Design a synchronous counter using T flip flops to count the sequence 0, 2, 3, 6, 5, 1, 0, 2, ... Write the excitation table and state diagram and logic diagram. (10 Marks)

OR

- 10 a. Explain Mealy and Moore model of clocked synchronous sequential circuit with the block diagram. (08 Marks)
 b. For the logic diagram given in Fig.Q10(b):
 i) Derive the excitation and output equations
 ii) Write the state equations
 iii) Construct transition table and state table
 iv) Draw the state diagram

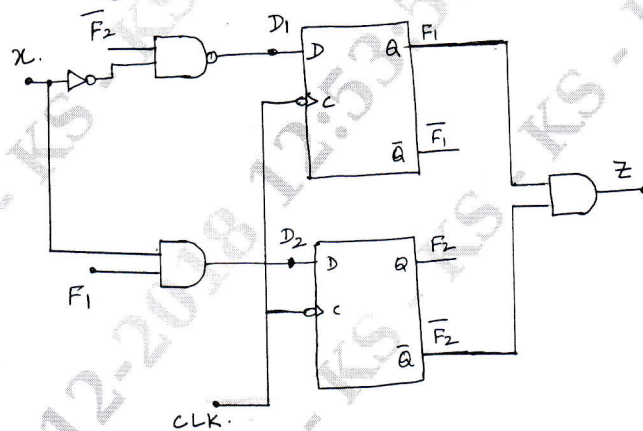


Fig.Q10(b)

(12 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC35

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

1. a. Reduce the Network shown in Fig Q1(a) to a single voltage source in series with a resistance using source shift and source transformation. (07 Marks)
- b. Use mesh analysis to determine the three mesh currents I_1 , I_2 and I_3 in the circuit show in Fig Q1(b). (05 Marks)
- c. Find current in 30Ω resistor using nodal analysis for the circuit shown in Fig Q1(c). (08 Marks)

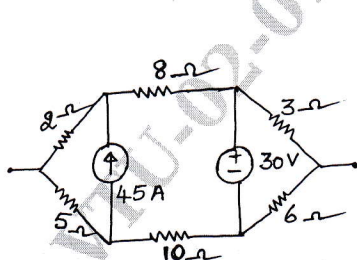


Fig Q1(a)

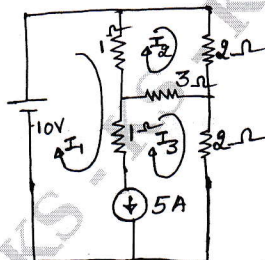


Fig Q1(b)

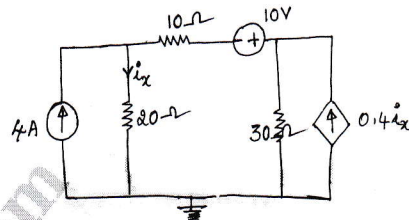


Fig Q1(c)

OR

2. a. Find the equivalent resistance between a and b using star delta transformation for the network shown in Fig Q2(a). (05 Marks)
- b. For the circuit shown in Fig Q2(b), determine I_x and other loop currents. (07 Marks)
- c. For the circuit shown in Fig Q2(c), determine all node voltages. (08 Marks)

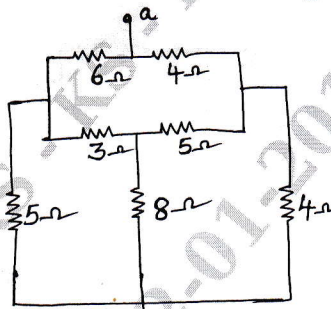


Fig 2(a)

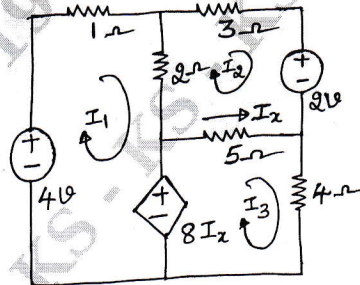


Fig 2(b)

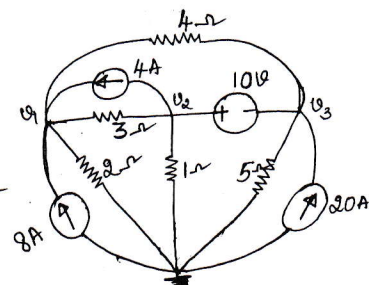


Fig 2(c)

Module-2

3. a. For the circuit shown in Fig Q3(a), find the current I_x using super position theorem. (07 Marks)
- b. Verify Reciprocity theorem by calculating 'I' for the network shown in Fig Q3(b). (05 Marks)
- c. Obtain the Thevenin's equivalent of the circuit shown in Fig Q 3(c) (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

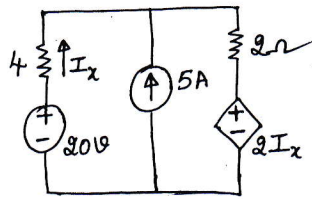


Fig Q3 (a)

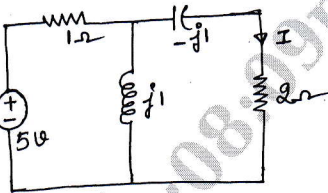


Fig Q3 (b)

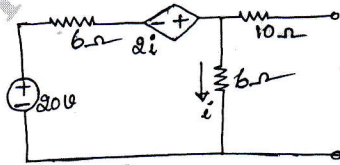


Fig Q3 Q(c)

OR

- 4 a. For the circuit shown in Fig Q4(a), find the current in $(6 + j8)\Omega$ impedance using Millman's theorem. (05 Marks)
- b. For the Network shown in Fig Q4(b), determine Norton's equivalent across A and B. Find the current through the impedance $(6 - j8)\Omega$ connected to the terminals A and B. (05 Marks)

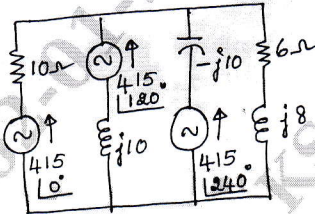


Fig Q4(a)

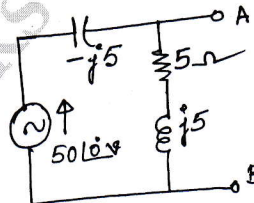


Fig Q4(b)

- c. State and prove maximum power transfer theorem for AC circuit, where both R_L and X_L are varying. (10 Marks)

Module-3

- 5 a. In the Network shown in Fig Q5(a), a steady state is reached with the switch K open. At $t = 0$, the switch K is closed. Obtain the initial values of (i) i_1 (ii) i_2 (iii) v_c (iv) $\frac{di_1}{dt}$ (v) $\frac{di_2}{dt}$ and $\frac{dv_c}{dt}$ at $t = \infty$. (10 Marks)
- b. For the given circuit in Fig Q5(b), find the value of the loop currents, their first derivatives and their 2nd derivatives, all evaluated at $t = 0^+$, given that $V_c(0^-) = 1$ volt, $i_2(0^-) = 0$ amp. At $t = 0$, sw_1 and sw_2 are closed. (10 Marks)

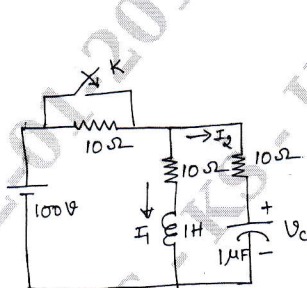


Fig Q5(a)

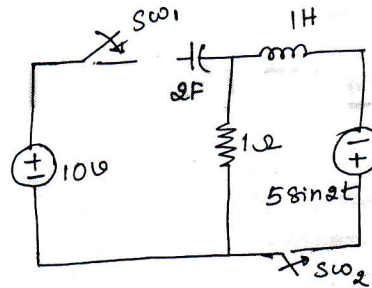


Fig Q5(b)

OR

- 6 a. In the circuit of Fig Q6(a), the source voltage is $v(t) = 50\sin 250t$. Using Laplace transforms, determine the current when switch K is closed at $t = 0$. (08 Marks)
- b. Synthesize the periodic waveform shown in Fig Q6(b) and find its Laplace transform and prove any formula used. (12 Marks)

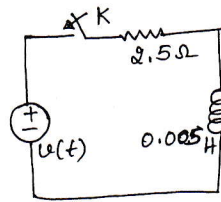


Fig Q6(a)

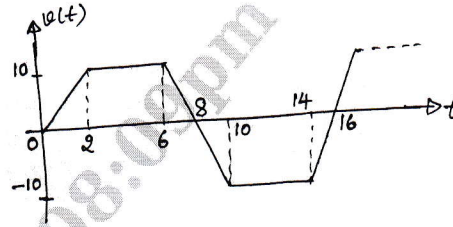


Fig Q6(b)

Module-4

- 7 a. Show that resonant frequency of series resonant circuit is equal to the geometric mean of two half power frequencies. (05 Marks)
- b. A coil is connected in series with a variable capacitor across $v(t) = 10 \cos 1000t$. The current is maximum when $c = 10 \mu\text{F}$. When $C = 12.5 \mu\text{F}$, the current is 0.707 times the maximum value. Find L, R, and Q of the coil. (08 Marks)
- c. A coil has resistance of 400Ω and inductance of $318 \mu\text{H}$. Find the capacitance of capacitor which when connected in parallel with the coil will produce resonance with a supply frequency of 1MHz. If a second capacitor of capacitance 23.42pF is connected in parallel with the first capacitor, find the frequency at which resonance will occur. (07 Marks)

OR

- 8 a. Derive the expression for the resonant frequency of the circuit shown in Fig Q8(a). Also show that the circuit will resonate at all frequencies if $R_L = R_c = \sqrt{\frac{L}{C}}$. (12 Marks)

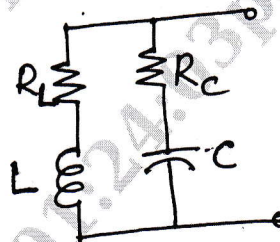


Fig Q8(a)

- b. A coil of 10Ω resistance 0.2H inductance is connected in parallel with a variable condenser across 220V , 50Hz supply. Determine: (i) Capacitance of condenser so that current drawn may be in phase with the supply voltage (ii) Effective impedance of the circuit (iii) Power absorbed at resonance (iv) Current magnification factor. (08 Marks)

Module-5

- 9 a. Z-parameters of a Network are obtained from an experiment. Explain how y-parameters and transmission parameter can be computed from the experimental data. (10 Marks)
- b. Find Z and Y parameters of the network shown in Fig Q9(b).

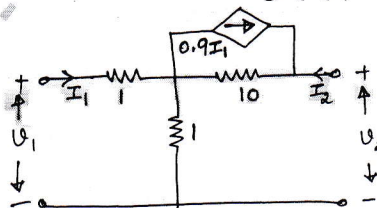


Fig Q9(b)

(10 Marks)

OR

- 10 a. Find Z and h-parameters for the network shown in Fig Q10(a).

(12 Marks)

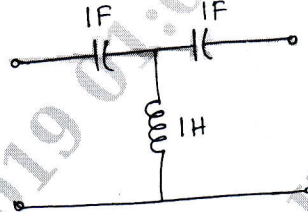


Fig Q10(a)

- b. Write a note on hybrid p's with its equivalent circuit.
c. Explain symmetry and reciprocal property of 2-port Networks.

(04 Marks)

(04 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC36

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Engineering Electromagnetics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. State and explain Coulomb's law in complete form. (06 Marks)
- b. Two particles having charges $2nc$ and $5nc$ are spaced $80cm$ apart. Determine the \vec{E} at a point is situated at a distance of $0.5m$ from each of the two particles. Use $\epsilon_r = 5$. (Use Bakelite medium). (06 Marks)
- c. Identical point charges of $3\mu c$ are located at the four corners of the square of $5cm$ side, find the magnitude of the force on any one charge? (08 Marks)

OR

- 2 a. Derive expression for E due to infinite line charge from first principle. (08 Marks)
- b. Two uniform line charges of density $4n c/m$ and $6n c/m$ lie in $x = 0$ plane at $y = +5m$ and $-6m$ respectively. Find E at $(4, 0, 5)^m$. (06 Marks)
- c. Define E and D , Hence establish the relation between D and E . (06 Marks)

Module-2

- 3 a. State and prove Gauss divergence theorem. (06 Marks)
- b. If $D = \frac{5r^2}{4} \hat{a}_r c/m^2$. (in spherical system) then evaluates both sides of the divergence theorem for the volume enclosed by $r = 4m$, and $\theta = \pi/4$ radians. (08 Marks)
- c. Prove that $\rho_v = \nabla \cdot D$. (06 Marks)

OR

- 4 a. Establish relation $E = -\nabla V$. (06 Marks)
- b. Electrical potential at an arbitrary point in free space is given as $V = (x+1)^2 + (y+2)^2 + (z+3)^2$ Volts at $p(2, 1, 0)$. Find :
i) V ii) \vec{E} iii) $|\vec{E}|$ iv) $|\vec{D}|$ v) ρ_v (08 Marks)
- c. Derive continuity of current equation. (06 Marks)

Module-3

- 5 a. Derive Laplace and Poisson's equations and write Laplace Equation in all 3 co-ordinate systems. (08 Marks)
- b. State and prove uniqueness theorem. (07 Marks)
- c. Calculate the numerical values for V and ρ_v at P in free space if $V = \frac{4yz}{x^2+1}$ at $P(1, 2, 3)$. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. An assembly of two concentric spherical shells is considered. The inner spherical shell is at a distance of 0.1m and is at a potential of 0 volts. The outer spherical shell is at a distance of 0.2m and at a potential of 100V. The medium between them is a free space. Find \vec{E} and \vec{D} using spherical co-ordinate system. (06 Marks)
- b. State and prove Ampers circuital law. (08 Marks)
- c. At a point P(x, y, z) the components of vector magnetic potential \vec{A} are given as
 $A_x = 4x + 3y + 2z$
 $A_y = 5x + 6y + 3z$ and
 $A_z = 2x + 3y + 5z$
 Determine \vec{B} at point P and state its nature. (06 Marks)

Module-4

- 7 a. Derive an expression for the force on a differential current element placed in a magnetic field and deduce the result for straight conductor in a uniform magnetic field. (08 Marks)
- b. A point charge $Q = 18\text{nc}$ has a velocity of 5×10^6 m/s in the direction $\vec{a}_v = 0.6\hat{a}_x + 0.75\hat{a}_y + 0.3\hat{a}_z$.
 Calculate the magnitude of the force exerted on the charge by the field
 i) $\vec{E} = -3\hat{a}_x + 4\hat{a}_y + 6\hat{a}_z$ K v/m
 ii) $\vec{B} = -3\hat{a}_x + 4\hat{a}_y + 6\hat{a}_z$ MT
 iii) \vec{B} & \vec{E} acting together. (06 Marks)
- c. State and explain Lorentz force equation. (06 Marks)

OR

- 8 a. Define : i) Magnetization ii) Permeability. (04 Marks)
- b. If $\vec{B} = 0.05 \times \hat{a}_y$ T in a material for which magnetic susceptibility $X_m = 2.5$. Find
 i) μ_r ii) μ iii) \vec{H} iv) \vec{M} v) \vec{J} vi) \vec{J}_b (08 Marks)
- c. Discuss the boundary conditions at the interface between two media of different permeabilities? (08 Marks)

Module-5

- 9 a. Derive Maxwell's Equations in point form and Integral form for Time varying fields. (08 Marks)
- b. For a lossy dielectric $\sigma = 5$ s/m, $\epsilon_r = 1$ the electric field intensity is $E = 100 \sin 10^{10} t$. Find J_c and J_d and frequency at which both have Equal Magnitudes. (04 Marks)
- c. Starting from Maxwell's Equation Derive the wave equation for a uniform plane wave travelling in free space. (08 Marks)

OR

- 10 a. State and prove Poynting theorem. (08 Marks)
- b. Deduce the expressions for α and β for a uniform plane wave propagation in good conducting medium. (06 Marks)
- c. Wet Marshy soil is characterized by $\sigma = 10^{-2}$ s/m, $\epsilon_r = 15$ and $\mu_r = 1$. At the frequencies 60Hz, 1 MHz, 100 MHz and 10 GHz indicate whether the soil may be considered a conducting dielectric or neither. (06 Marks)