

CBCGS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15MAT31

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Engineering Mathematics - III

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. An alternating current after passing through a rectifier has the form,

$$I = \begin{cases} I_0 \sin x & \text{for } 0 < x < \pi \\ 0 & \text{for } \pi < x < 2\pi \end{cases}$$

where I_0 is the maximum current and the period is 2π . Express I as a Fourier series.

(08 Marks)

- b. Determine the constant term and the first cosine and sine terms of the Fourier series expansion of y from the following data:

(08 Marks)

x^0	0	45	90	135	180	225	270	315
y	2	1.5	1	0.5	0	0.5	1	1.5

OR

- 2 a. Obtain the Fourier series expansion of the function, $f(x) = |x|$ in $(-\pi, \pi)$ and hence deduce that,

$$\frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots = \frac{\pi^2}{8}$$

(06 Marks)

- b. Find the Fourier series expansion of the function,

$$f(x) = \begin{cases} \pi x & \text{in } 0 \leq x \leq 1, \\ \pi(2-x) & \text{in } 1 \leq x \leq 2 \end{cases}$$

(05 Marks)

- c. The following table gives the variations of periodic current over a period.

t(sec)	0	$\frac{T}{6}$	$\frac{T}{3}$	$\frac{T}{2}$	$\frac{2T}{3}$	$\frac{5T}{6}$	T
A(amplitude)	1.98	1.30	1.05	1.3	-0.88	-0.25	1.98

Show by harmonic analysis that there is a direct current part of 0.75 amp in the variable current and obtain the amplitude of first harmonic.

(05 Marks)

Module-2

- 3 a. Find the complex Fourier transform of the function $f(x) = \begin{cases} 1 & \text{for } |x| \leq a \\ 0 & \text{for } |x| > a \end{cases}$. Hence evaluate

$$\int_0^{\infty} \frac{\sin x}{x} dx.$$

(06 Marks)

- b. Find the Fourier sine transform of $\frac{e^{-ax}}{x}$.

(05 Marks)

- c. Compute the inverse z-transforms of $\frac{3z^2 + 2z}{(5z-1)(5z+2)}$.

(05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Find the z-transform of $e^{-an}n + \sin n \frac{\pi}{4}$. (06 Marks)
- b. Solve $y_{n+2} + 6y_{n+1} + 9y_n = 2^n$ with $y_0 = y_1 = 0$ using z-transform. (05 Marks)
- c. Find the Fourier cosine transform of, $f(x) = \begin{cases} 4x & 0 < x < 1 \\ 4-x & 1 < x < 4. \\ 0 & x > 4 \end{cases}$. (05 Marks)

Module-3

- 5 a. Find the Correlation coefficient and equations of regression lines for the following data:
- | | | | | | |
|---|---|---|---|---|---|
| x | 1 | 2 | 3 | 4 | 5 |
| y | 2 | 5 | 3 | 8 | 7 |
- (06 Marks)
- b. Fit a straight line to the following data:
- | | | | | | |
|---|---|-----|-----|-----|-----|
| x | 0 | 1 | 2 | 3 | 4 |
| y | 1 | 1.8 | 3.3 | 4.5 | 6.3 |
- (05 Marks)
- c. Find a real root of the equation $xe^x = \cos x$ correct to three decimal places that lies between 0.5 and 0.6 using Regula-falsi method. (05 Marks)

OR

- 6 a. The following regression equations were obtained from a correlation table.
 $y = 0.516x + 33.73$
 $x = 0.516y + 32.52$
 Find the value of (i) Correlation coefficient (ii) Mean of x's (iii) Mean of y's. (06 Marks)
- b. Fit a second degree parabola to the following data:
- | | | | | | | | |
|---|-----|-----|-----|-----|-----|-----|-----|
| x | 1.0 | 1.5 | 2.0 | 2.5 | 3.0 | 3.5 | 4.0 |
| y | 1.1 | 1.3 | 1.6 | 2.0 | 2.7 | 3.4 | 4.1 |
- (05 Marks)
- c. Use Newton-Raphson's method to find a real root of $x \sin x + \cos x = 0$ near $x = \pi$, carry out three iterations. (05 Marks)

Module-4

- 7 a. The following data gives the melting point of an alloy of lead and zinc, where t is the temperature in °C and P is the percentage of lead in the alloy:
- | | | | | |
|----|-----|-----|-----|-----|
| P% | 60 | 70 | 80 | 90 |
| t | 226 | 250 | 276 | 304 |
- Find the melting point of the alloy containing 84% of lead, using Newton's interpolation formula. (06 Marks)
- b. Apply Lagrange's interpolation formula to find a polynomial which passes through the points (0, -20), (1, -12), (3, -20) and (4, -24) (05 Marks)
- c. Find the approximate value of $\int_0^{\frac{\pi}{2}} \sqrt{\cos \theta} d\theta$ by Simpson's $\frac{3}{8}$ rule by dividing it into 6 equal parts. (05 Marks)

OR

- 8 a. From the following table :

x°	10	20	30	40	50	60
$\cos x$	0.9848	0.9397	0.8660	0.7660	0.6428	0.5

- b. Calculate $\cos 25^\circ$ using Newton's forward interpolation formula. (06 Marks)
- c. Use Newton's divided difference formula and find $f(6)$ from the following data:

x	5	7	11	13	17
$f(x)$	150	392	1452	2366	5202

- (05 Marks)
- c. Evaluate $\int_0^1 \frac{dx}{1+x}$ using Weddle's rule by taking equidistant ordinates. (05 Marks)

Module-5

- 9 a. Find the area between the parabolas $y^2 = 4x$ and $x^2 = 4y$ with the help of Green's theorem in a plane. (06 Marks)
- b. Solve the variational problem $\delta \int_0^1 (12xy + y'^2) dx = 0$ under the conditions $y(0) = 3$, $y(1) = 6$. (05 Marks)
- c. Prove that the shortest distance between two points in a plane is along the straight line joining them. (05 Marks)

OR

- 10 a. A cable hangs freely under gravity from the fixed points. Show that the shape of the curve is a catenary. (06 Marks)
- b. Use Stoke's theorem to evaluate for $\vec{F} = (x^2 + y^2)\mathbf{i} - 2xy\mathbf{j}$ taken around the rectangle bounded by the lines $x = \pm a$, $y = 0$, $y = b$. (05 Marks)
- c. Evaluate $\iiint_S (yzi + xzj + xyk) \cdot \hat{n} ds$ where S is the surface of the sphere $x^2 + y^2 + z^2 = a^2$ in the first octant. (05 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15MATDIP31

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Additional Mathematics – I

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Find the modulus and amplitude of $\frac{(3 + \sqrt{2}i)^2}{1 + 2i}$. (06 Marks)
- b. Find the cube root of $(1 - i)$. (05 Marks)
- c. Prove that $\left(\frac{1 + \sin \theta + i \cos \theta}{1 + \sin \theta - i \cos \theta}\right)^n = \cos\left(n\frac{\pi}{2} - n\theta\right) + i \sin\left(n\frac{\pi}{2} - n\theta\right)$. (05 Marks)

OR

- 2 a. For any three vector a, b, c show that $\left[\begin{matrix} \vec{a} & \vec{b} & \vec{c} \\ \vec{a} + \vec{b} & \vec{b} + \vec{c} & \vec{c} + \vec{a} \end{matrix}\right] = 2 \left[\begin{matrix} \vec{a} & \vec{b} & \vec{c} \end{matrix}\right]$ (06 Marks)
- b. Find the value of λ so that the vectors $\vec{a} = 2\hat{i} - 3\hat{j} + \hat{k}$, $\vec{b} = \hat{i} + 2\hat{j} - 3\hat{k}$ and $\vec{c} = \hat{j} + \lambda\hat{k}$ are coplanar. (05 Marks)
- c. Find the angle between the vectors $\vec{a} = 5\hat{i} - \hat{j} + \hat{k}$ and $\vec{b} = 2\hat{i} - 3\hat{j} + 6\hat{k}$ (05 Marks)

Module-2

- 3 a. Find the n^{th} derivative of $\cos x \cos 2x \cos 3x$. (06 Marks)
- b. If $y = a \cos(\log x) + b \sin(\log x)$, prove that $x^2 y_{n+2} + (2n+1)xy_{n+1} + (n^2+1)y_n = 0$. (05 Marks)
- c. Find the angle between the radius vector and tangents for the curve $r^2 \cos 2\theta = a^2$ (05 Marks)

OR

- 4 a. If $u = e^{ax+by} + (ax - by)$ prove that $b \frac{\partial u}{\partial x} + a \frac{\partial u}{\partial y} = 2abu$. (06 Marks)
- b. If $u = \sin^{-1}\left(\frac{x^2 + y^2}{x - y}\right)$ prove that $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \tan u$. (05 Marks)
- c. If $x = u(1 - v)$, $y = uv$. Find $\frac{\partial(x, y)}{\partial(u, v)}$. (05 Marks)

Module-3

- 5 a. Obtain the reduction formula for $\int_0^{\frac{\pi}{2}} \cos^n x dx$ ($n > 0$). (06 Marks)
- b. Evaluate $\int_0^1 x^6 \sqrt{1-x^2} dx$. (05 Marks)
- c. Evaluate $\int_0^1 \int_0^1 \int_0^y xyz dx dy dz$. (05 Marks)

OR

- 6 a. Obtain the reduction formula for $\int_0^{\frac{\pi}{2}} \sin^n x dx$, $n > 0$. (06 Marks)
- b. Evaluate $\int_0^a x^2 (a^2 - x^2)^{\frac{3}{2}} dx$. (05 Marks)
- c. Evaluate $\int_0^1 \int_0^{\sqrt{x}} xy dy dx$. (05 Marks)

Module-4

- 7 a. A particle moves along a curve $x = e^{-t}$, $y = 2 \cos 3t$, $z = 2 \sin 3t$ where t is the time. Determine the component of velocity and acceleration vector at $t = 0$ in the direction of $\hat{i} + \hat{j} + \hat{k}$. (08 Marks)
- b. Find the value of the constant a, b , such that $\vec{F} = (axy + z^3)\hat{i} + (3x^2 - z)\hat{j} + (bxz^2 - y)\hat{k}$ is irrotational. (08 Marks)

OR

- 8 a. If $\vec{F} = (x + y + 1)\hat{i} + \hat{j} - (x + y)\hat{k}$ show that $\vec{F} \cdot \text{curl} \vec{F} = 0$. (06 Marks)
- b. If $\phi(x, y, z) = x^3 + y^3 + z^3 - 3xyz$ find $\nabla \phi$ at $(1, -1, 2)$. (05 Marks)
- c. Find the directional derivative $\phi(x, y, z) = x^2yz + 4xz^2$ at $(1, -2, -1)$ in the direction of $2\hat{i} - \hat{j} - 2\hat{k}$. (05 Marks)

Module-5

- 9 a. Solve $\frac{dy}{dx} = \frac{y}{x - \sqrt{xy}}$. (06 Marks)
- b. Solve $ye^{xy} dx + (xe^{xy} + 2y) dy = 0$ (05 Marks)
- c. $\frac{dy}{dx} - \frac{2y}{x} = x + x^2$. (05 Marks)

OR

- 10 a. Solve $\frac{dy}{dx} = \frac{y}{x} + \sin\left(\frac{y}{x}\right)$. (06 Marks)
- b. Solve $(y^3 - 3x^2y) dx - (x^3 - 3xyz) dy = 0$ (05 Marks)
- c. Solve $(1 + y^2) dx + (x - \tan^{-1} y) dy = 0$ (05 Marks)

CBCGS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC32

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Define h parameters using two port systems. (05 Marks)
- b. Derive expressions for input impedance, output impedance and voltage gain for common emitter fixed bias configuration using re model. (07 Marks)
- c. Find Z_i , Z_o , A_v and A_i for the network shown in Fig.Q.1(c). Given data $h_{fb} = -0.99$, $h_{ib} = 14.3\Omega$, $h_{ob} = 0.5 \mu A/v$. (04 Marks)

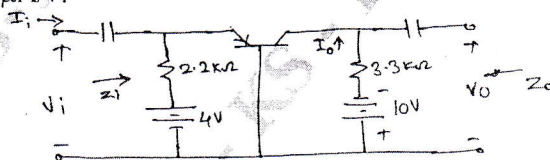


Fig.Q.1(c)

OR

- 2 a. Explain hybrid π model. (04 Marks)
- b. Find r_e , Z_i , Z_o and A_v for the circuit shown in Fig.Q.2(b). Given data $B = 90$, $r_o = 50k\Omega$. (05 Marks)

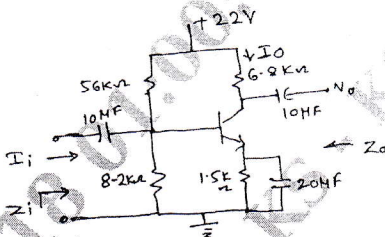


Fig.Q.2(b)

- c. Derive the expressions for Z_i , Z_o , A_v and A_i for fixed bias configuration using approximate $C\pi$ hybrid equivalent model. (07 Marks)

Module-2

- 3 a. List the differences between JFET and MOSFET. (04 Marks)
- b. Explain with neat sketches, operation and characteristics of n-channel E-MOSFET. (08 Marks)
- c. Find: i) input impedance ii) output impedance iii) voltage gain for the circuit shown in Fig.Q.3(c). Given data $g_m = 2ms$, $r_d = 50K\Omega$. (04 Marks)

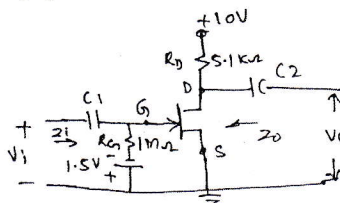


Fig.Q.3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Find transconductance and drain current for the JFET if $I_{DSS} = 20\text{mA}$, $V_P = -5\text{V}$, $V_{GS} = -4\text{V}$ and $g_{m0} = 4\text{ms}$. (04 Marks)
- b. Derive an expressions for Z_i , Z_o and A_v using small signal JFET amplifier under fixed bias configuration. (07 Marks)
- c. Sketch the following circuit diagrams:
- JFET ac equivalent model of source follower
 - Cascaded FET amplifier. (05 Marks)

Module-3

- 5 a. An amplifier rated at a 40W output is connected to a 10Ω speaker, Find:
- Input power required for full output if power gain is 25dB
 - Input voltage for rated output if the amplifier voltage gain is 40dB. (04 Marks)
- b. Explain high frequency response of FET amplifier. (07 Marks)
- c. Explain multistage frequency effects. (05 Marks)

OR

- 6 a. Derive an expressions for Miller input and output capacitor. (06 Marks)
- b. Determine A_v , Z_i and A_{v_s} for the low frequency response of the BJT amplifier circuit shown in Fig.Q.6(b). Assume $r_0 = \infty$. (06 Marks)

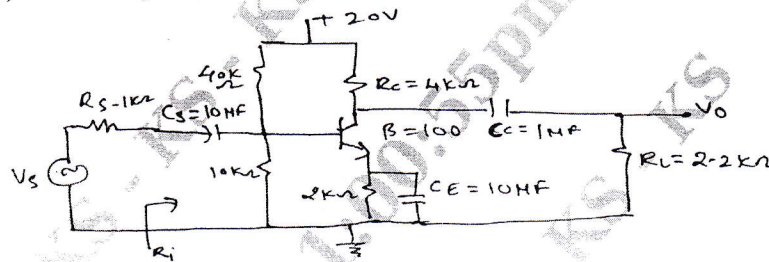


Fig.Q.6(b)

- c. Draw the circuit diagram of high frequency response of BJT amplifier under CE mode with capacitances. (04 Marks)

Module-4

- 7 a. List the conditions for sustained oscillations. (04 Marks)
- b. Determine the voltage gain, input impedance and output impedance with feedback for series voltage feedback having $A = -100$, $R_i = 10\text{k}\Omega$ and $R_o = 20\text{k}\Omega$ for feedback factor $\beta = -0.1$. (05 Marks)
- c. Explain with neat circuit diagram the operation of colpitt oscillator. (07 Marks)

OR

- 8 a. Show that gain with feedback in voltage series feedback system reduced by a factor $(1 + AB)$. (05 Marks)
- b. Explain the operation of FET RC phase oscillator with neat circuit diagram. (06 Marks)
- c. Design the RC elements of a Wein bridge oscillator for the operation at $f = 10\text{kHz}$ and draw the oscillator circuit diagram. (05 Marks)

Module-5

- 9 a. Define class A, class B, class C and class D power amplifiers. (04 Marks)
 b. Calculate the output voltage and the zener current for the regulator shown in Fig.Q9(b) for $R_L = 1K\Omega$. (04 Marks)

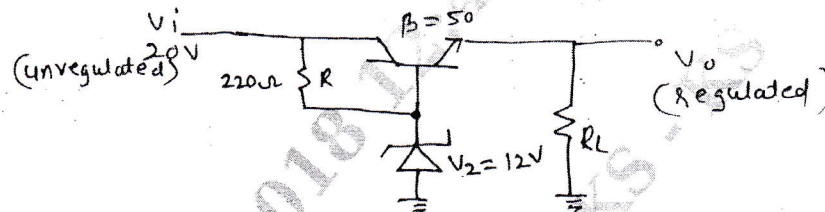


Fig.Q.9(b)

- c. Explain with neat diagram and waveforms class B push pull power amplifier. (08 Marks)

OR

- 10 a. Compare the series and shunt voltage regulators. (04 Marks)
 b. Define the following:
 i) Cross over distortion
 ii) Harmonic distortion
 iii) Percentage load regulation
 iv) Amplifiers efficiency (04 Marks)
 c. Calculate input power, output power and efficiency of the series fed class A power amplifier circuit shown in Fig.Q10(c). (08 Marks)

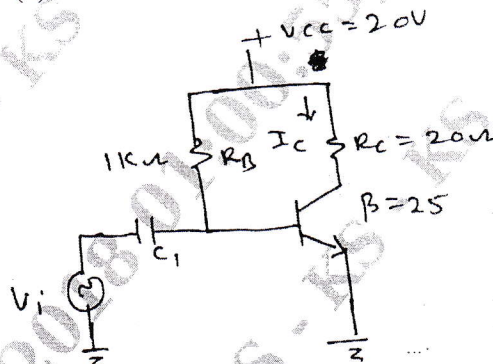


Fig.Q.10(c)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC33

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing
ONE full question from each module.

Module-1

- Define combinational logic. Design a combinational circuit which takes two, 2 bit binary numbers as its input and generates an output equal to 1, when the sum of the two numbers is even. (10 Marks)
 - Simplify using Karnaugh map. Write the Boolean equation and realize using NAND gates.
 $D = f(w, x, y, z) = \Sigma m(0, 2, 4, 6, 8) + \Sigma d(10, 11, 12, 13, 14, 15)$. (06 Marks)

OR

- Define canonical SOP and canonical POS. Expand $f = (\bar{a} + b + c)(a + c + \bar{d})$ into canonical POS. (04 Marks)
 - Solve using Quine-McCluskey tabulation method,
 $f(a, b, c, d) = \Sigma m(0, 1, 4, 5, 9, 10, 12, 14, 15) + \Sigma \phi(2, 8, 13)$
Obtain the minimal form of the given function. Verify the result using k-map. (12 Marks)

Module-2

- Define decoder. Implement full subtractor using a decodes. Write the truth table. (08 Marks)
 - Compare ripple carry adder and look ahead carry adder. Explain the circuit and operation of a 4 bit binary adder with look ahead carry. (08 Marks)

OR

- Design and implement one bit comparator. (04 Marks)
 - Implement the multiple functions :
 $f_1(a, b, c, d) = \Sigma(0, 4, 8, 10, 14, 15)$ and
 $f_2(a, b, c, d) = \Sigma(3, 7, 9, 13)$
using two 3 to 8 decoders, i.e. 74138 ICs. (06 Marks)
 - Implement full adder circuit using 8 : 1 multiplexer. (06 Marks)

Module-3

- What is gated SR Latch? Explain the operation of gated SR Latch, with a logic diagram, truth table and logic symbol. (08 Marks)
 - Derive the characteristic equation of SR, JK, D and T flip-flops with the help of function tables. (08 Marks)

OR

- Explain the operation of a switch debouncer built using SR Latch. Draw the supporting waveforms. (04 Marks)
 - Explain 0s and 1s catching problem of Master Slave JK flip flop with waveform. Suggest the solution for this problem. (04 Marks)
 - What is edge triggered flip flop? With a neat circuit diagram, explain the operation of positive edge triggered D flip flop, using NAND gates. (08 Marks)

Module-4

- 7 a. With the help of neat diagram, explain PISO and PIPO operation of unidirectional shift registers. (08 Marks)
 b. Design a 4 bit binary ripple 'UP' counter using negative edge triggered JK flip flop. Show the up counter execution with the help of timing diagram. (08 Marks)

OR

- 8 a. Implement a Mod 8 twisted ring counter using D flip flops. Give the counting sequence and decoding gate inputs. (06 Marks)
 b. Design a synchronous MOD-6 counter using JK flip flop for the following count sequence 0, 2, 3, 6, 5, 1 and repeat. Write the transition table, logic equations and the counter implementation diagram. (10 Marks)

Module-5

- 9 a. Compare Mealy and Moore sequential circuit models with suitable example. (04 Marks)
 b. For the logic diagram shown in Fig.Q9(b), write the state and output equations. Give the transition table and the state diagram. (12 Marks)

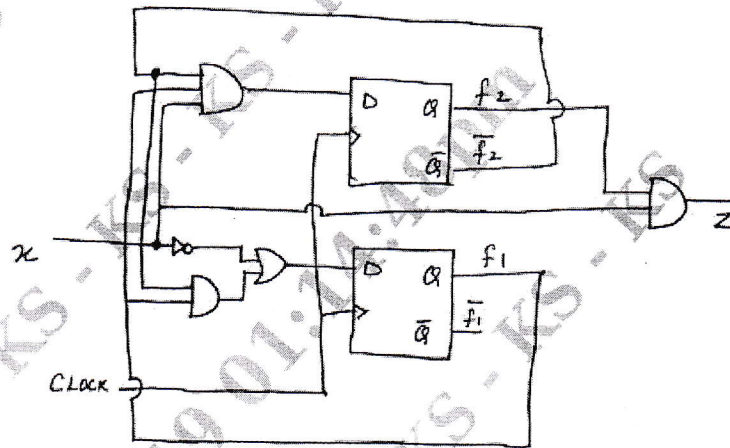


Fig.Q9(b)

OR

- 10 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
 b. How to convert a Mealy machine to a Moore machine? (02 Marks)
 c. A sequential circuit has one input and one output. The state diagram is shown in Fig.Q10(c). Design a sequential circuit using D flip flop. (08 Marks)

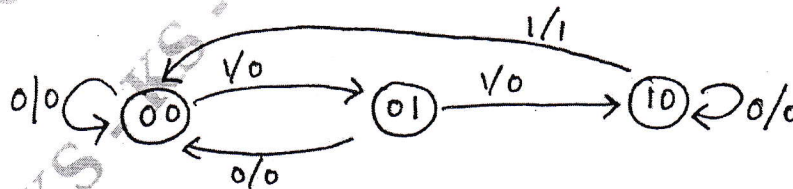


Fig.Q10(c)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC34

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Network Analysis

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Reduce the network shown in Fig.Q1(a) to a single voltage source in series with a resistance using source shift and source transformations. (08 Marks)

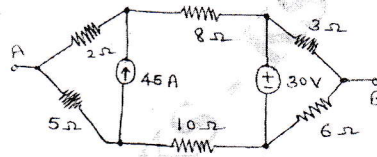


Fig.Q1(a)

- b. Using star/delta transformation, determine the resistance between M and N for the network shown in Fig.Q1(b). (08 Marks)

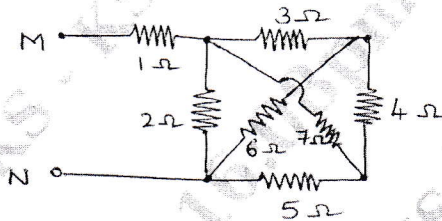


Fig.Q1(b)

OR

- 2 a. Find the power delivered by the dependent voltage source in the circuit shown in Fig.Q2(a) by Mesh current method. (06 Marks)

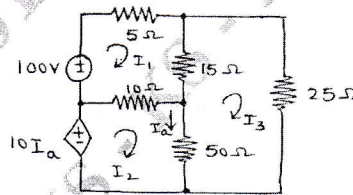


Fig.Q2(a)

- b. Define super Mesh and super node. (02 Marks)
c. Use the node-voltage method to find the power developed by the 20V source in the circuit shown in Fig.Q2(c). (08 Marks)

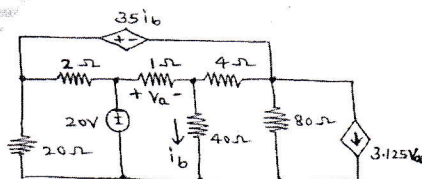


Fig.Q2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. Use superposition theorem to find v_x in the circuit shown in Fig.Q3(a). (08 Marks)

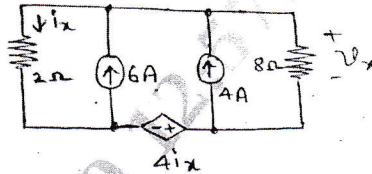


Fig.Q3(a)

- b. State and prove reciprocity theorem. (08 Marks)

OR

- 4 a. State and prove Thevenin's theorem. (06 Marks)
 b. Find the Norton's equivalent circuit across AB terminals for the network shown in Fig.Q4(b) and hence determine current through 5Ω resistor. (06 Marks)

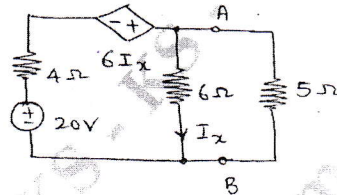


Fig.Q4(b)

- c. Find the value of Z_L for which Maximum Power transfer occurs in the circuit shown in Fig.Q4(c). (04 Marks)

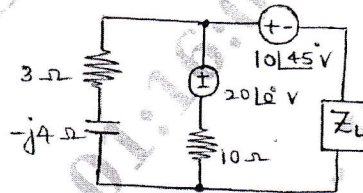


Fig.Q4(c)

Module-3

- 5 a. In the network shown in Fig.Q5(a), the switch k is closed at $t = 0$. Find the values of i_1 , i_2 $\frac{di_1}{dt}$ and $\frac{d^2i_2}{dt^2}$ at $t = 0$. (08 Marks)

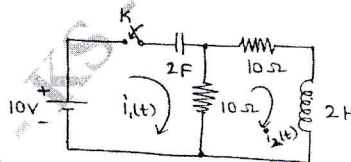


Fig.Q5(a)

- b. In the circuit shown in Fig.Q5(b), the capacitor C_1 is charged to a voltage V_0 at $t = 0$, the switch is closed. Solve for the charge as a function of time. (08 Marks)

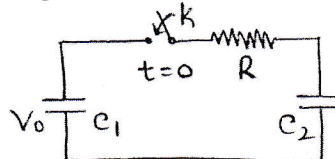


Fig.Q5(b)

OR

- 6 a. State and prove the following : i) Initial value theorem ii) Final value theorem. (08 Marks)
 b. For the waveform shown in Fig.Q6(b), the equation of the waveforms is $\sin(t)$ from 0 to π , and $-\sin(t)$ from π to 2π , show that the Laplace transform of this waveform is :

$$F(s) = \frac{1}{s^2 + 1} \cot h\left(\frac{\pi s}{2}\right).$$

(08 Marks)

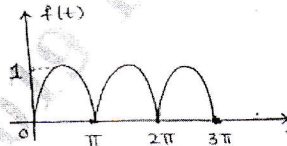


Fig.Q6(b)

Module-4

- 7 a. Define the following terms :
 i) Resonance ii) Bandwidth. (02 Marks)
 b. Prove that $f_0 = \sqrt{f_1 f_2}$ where f_1 and f_2 are the two half power frequencies of a resonant circuits. (06 Marks)
 c. A series RLC circuit has $R = 2\Omega$, $L = 2$ mH and $C = 10\mu\text{f}$ calculate Q-factor, bandwidth, Resonant frequency and half power frequencies f_1 and f_2 . (08 Marks)

OR

- 8 a. Show that a two-branch parallel circuit is resonant at all frequencies if $R_L = R_C = \sqrt{\frac{L}{C}}$. (08 Marks)
 b. Find the values of L for which the circuit given in Fig.Q8(b) resonates at $\omega = 5000$ r/sec. (08 Marks)

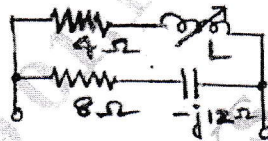


Fig.Q8(b)

Module-5

9. a. Express Z - parameters in terms of Y-parameters. (08 Marks)
 b. Obtain ABCD parameters in terms of impedance parameters (Z) and hence show that $AD - BC = 1$. (08 Marks)

OR

- 10 a. For the network shown in Fig.Q10(a), contains an voltage controlled source and current controlled source, for the elemental values specified, determine Z and Y parameters. (08 Marks)

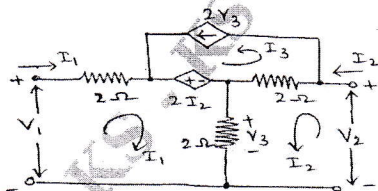


Fig.Q10(a)

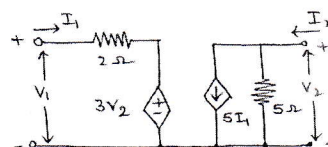


Fig.Q10(b)

- b. Determine transmission parameters for the network shown in Fig.Q10(b). (08 Marks)

CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC36

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018

Engineering Electromagnetics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. State and explain Coulomb's law in vector form. (05 Marks)
- b. Find the electric field \vec{E} at origin, if the following charge distributions are present in free space:
- Point charge 12 nC at P(2, 0, 6).
 - Uniform line charge of linear charge density 3 nC/m at $x = 2, y = 3$.
 - Uniform surface charge of density $P_s = 0.2 \text{ nC/m}^2$ at $x = 2$. (06 Marks)
- c. Define volume charge density. Also find the total charge within each of the indicated volumes.
- $0 \leq \rho \leq 0.1, 0 \leq \phi \leq \pi, 2 \leq z \leq 4; \rho_v = \rho^2 z^2 \sin(0.6\phi)$
 - Universe : $\rho_v = \frac{e^{-2r}}{r^2}$ (05 Marks)

OR

- 2 a. Define Electric flux and flux density. (04 Marks)
- b. Given a 60 μC point charge located at the origin, find the total electric flux passing through:
- That portion of the sphere $\gamma = 26 \text{ cm}$ bounded by $0 < \theta < \frac{\pi}{2}$ and $0 < \phi < \frac{\pi}{2}$.
 - The closed surface defined by $\rho = 26 \text{ cm}$ and $z = \pm 26 \text{ cm}$.
 - The plane $z = 26 \text{ cm}$. (07 Marks)
- c. Derive the expression for \vec{E} due to infinite line charge of charge density $\rho_L \text{ (C/m)}$. (05 Marks)

Module-2

- 3 a. State and prove Gauss law for point charge. (05 Marks)
- b. State and prove divergence theorem. (05 Marks)
- c. In each of the following parts, find value for $\text{div } \vec{D}$ at the point specified:
- $\vec{D} = (2xyz - y^2)\vec{a}_x + (x^2z - 2xy)\vec{a}_y + x^2y\vec{a}_z \text{ c/m}^2$ at $P_A(2, 3, -1)$.
 - $\vec{D} = 2\rho z^2 \sin^2 \phi \vec{a}_\rho + \rho z^2 \sin 2\phi \vec{a}_\phi + 2\rho^2 z \sin^2 \phi \vec{a}_z \text{ c/m}^2$ at $P_B(\rho = 2, \phi = 110^\circ, z = -1)$. (06 Marks)

OR

- 4 a. Define potential difference and absolute potential. (04 Marks)
- b. A point charge of 6 nC is located at origin in free space, find potential of point p, if p is located at (0.2, -0.4, 0.4) and
- $V = 0$ at infinity
 - $V = 0$ at (1, 0, 0)
 - $V = 20 \text{ V}$ at (-0.5, 1, -1) (06 Marks)
- c. Derive point form of continuity equation for current. (06 Marks)

Module-3

- 5 a. Derive the expression for Poisson's and Laplace's equation. (05 Marks)
 b. Two plates of parallel plate capacitors are separated by distance 'd' and maintained at potential zero and V_0 respectively. Assuming negligible fringing effect, determine potential at any point between the plates. (06 Marks)
 c. State and prove uniqueness theorem. (05 Marks)

OR

- 6 a. State and explain Biot-Savart law. (06 Marks)
 b. Find the magnetic flux density at the centre 'O' of a square of sides equal to 5m and carrying 10 amperes of current. (06 Marks)
 c. At a point p(x, y, z), the components of vector magnetic potential \bar{A} are given as $A_x = 4x + 3y + 2z$, $A_y = 5x + 6y + 3z$ and $A_z = 2x + 3y + 5z$. Determine \bar{B} at point P. (04 Marks)

Module-4

- 7 a. Derive Lorentz force equation. (05 Marks)
 b. Derive an expression for the force on a differential current element placed in a magnetic field. (06 Marks)
 c. A conductor 4m long lies along the y-axis with a current of 10 amps in the \bar{a}_y direction. Find the force on the conductor if the field is $\bar{B} = 0.005 \bar{a}_x$ Telsa. (05 Marks)

OR

- 8 a. Define: i) Magnetization, ii) Permeability. (04 Marks)
 b. Find the magnetization in a magnetic material where
 i) $\mu = 1.8 \times 10^5$ (H/m) and 120 (A/m)
 ii) $\mu_r = 22$, there are 8.3×10^{28} atoms/m³ and each atom has a dipole moment of 4.5×10^{-27} (A/m²) and
 iii) $B = 300 \mu\text{T}$ and $\chi_m = 15$. (06 Marks)
 c. Discuss the boundary conditions at the interface between two media of different permeabilities. (06 Marks)

Module-5

- 9 a. State and explain Faraday's law of electromagnetic induction. (04 Marks)
 b. Find the frequency at which conduction current density and displacement current are equal in a medium with $\sigma = 2 \times 10^{-4}$ U/m and $\epsilon_r = 81$. (06 Marks)
 c. List Maxwell's equations in point form and integral form. (06 Marks)

OR

- 10 a. Obtain solution of the wave equation for a uniform plane wave in free space. (06 Marks)
 b. State and prove Poynting theorem. (06 Marks)
 c. The depth of penetration in a certain conducting medium is 0.1 m and the frequency of the electromagnetic wave is 1.0 MHz. Find the conductivity of the conducting medium. (04 Marks)

* * * * *