

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18MAT31

## Third Semester B.E. Degree Examination, Aug./Sept.2020 Transform Calculus, Fourier Series and Numerical Techniques

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Find  $L\{e^{-2t}t \cos 2t\}$ . (06 Marks)
- b. Express the function in terms of unit step function and hence find Laplace transform of :
- $$f(t) = \begin{cases} 1 & 0 \leq t \leq 1 \\ t & 1 < t \leq 2. \\ t^2 & t > 2 \end{cases}$$
- (07 Marks)
- c. Solve the equation  $y''(t) + 3y'(t) + 2y(t) = 0$  under the condition  $y(0) = 1, y'(0) = 0$ . (07 Marks)

OR

- 2 a. Find :
- i)  $L^{-1}\left\{\frac{s+3}{s^2-4s+13}\right\}$  ii)  $L^{-1}\left\{\log \frac{(s^2+1)}{s(s+1)}\right\}$ . (06 Marks)
- b. Find  $L^{-1}\left\{\frac{s^2}{(s^2+a^2)^2}\right\}$  using convolution theorem. (07 Marks)
- c. A periodic function of period  $2a$  is defined by
- $$f(t) = \begin{cases} E & 0 \leq t \leq a \\ -E & a < t \leq 2a \end{cases}$$

Where  $E$  is a constant and show that  $\text{trim } L\{f(t)\} = \frac{E}{S} \tan h\left(\frac{as}{2}\right)$ . (07 Marks)

### Module-2

- 3 a. Express  $f(x) = x^2$  as a Fourier series in the interval  $-\pi < x < \pi$ . Hence deduce that
- $$\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \frac{1}{4^2} + \dots = \frac{\pi^2}{12}$$
- (07 Marks)
- b. Obtain the Fourier series expression of  $f(x) = \begin{cases} \pi x & 0 < x < 1 \\ \pi(2-x) & 1 < x < 2 \end{cases}$ . (07 Marks)
- c. Obtain the half range cosine series for the function  $f(x) = (x-1)^2, 0 \leq x \leq 1$ . (06 Marks)

OR

- 4 a. Obtain the Fourier series of  $f(x) = \left(\frac{\pi-x}{2}\right)$   $0 < x < 2\pi$ . Hence deduce that

$$1 - \frac{1}{3} + \frac{1}{5} - \frac{1}{7} + \dots = \frac{\pi}{4}. \quad (07 \text{ Marks})$$

- b. Obtain the half range cosine series of  $f(x) = x \sin x$   $0 \leq x \leq \pi$ . (07 Marks)  
 c. Express  $f(x)$  as a Fourier series upto first harmonic.

x	0	1	2	3	4	5
f(x)	4	8	15	7	6	2

(06 Marks)

**Module-3**

- 5 a. Find the Fourier cosine transform of

$$f(x) = \begin{cases} x & \text{for } 0 < x < 1 \\ (2-x) & \text{for } 1 < x < 2. \\ 0 & \text{for } x > 2 \end{cases} \quad (07 \text{ Marks})$$

- b. Find the Fourier transform by  $f(x) = e^{-|x|}$ . (07 Marks)

- c. Obtain the inverse Z - transform by  $u(z) = \frac{z}{(z-2)(z-3)}$ . (06 Marks)

OR

- 6 a. Find the Fourier transform by

$$f(x) = \begin{cases} 1-|x| & |x| < 1 \\ 0 & |x| > 1 \end{cases}$$

and show that  $\int_0^{\infty} \frac{\sin^2 t}{t^2} dt = \frac{\pi}{2}$ . (07 Marks)

- b. Find the z-transform of: i)  $\cos n\theta$  ii)  $\sin n\theta$ . (06 Marks)

- c. Solve using Z -transform  $u_{n+2} - 4u_n = 0$  given that  $u_0 = 0$  and  $u_1 = 2$ . (07 Marks)

**Module-4**

- 7 a. Using Taylor's series method solve  $y(x) = x + y$ ,  $y(0) = 1$  then find  $y$  at  $x = 0.1, 0.2$  consider upto 4<sup>th</sup> degree. (07 Marks)

- b. Solve  $y'(x) = 1 + \frac{y}{z}$ ,  $y(1) = 2$  then find  $y(1.2)$  with  $n = 0.2$  using modified Euler's method. (06 Marks)

- c. Solve  $y'(x) = x - y^2$  and the data is  $y(0) = 0$ ,  $y(0.2) = 0.02$ ,  $y(0.4) = 0.0795$ ,  $y(0.6) = 0.1762$  then find  $y(0.8)$  by applying Milne's method and applying corrector formula twice. (07 Marks)

OR

- 8 a. Solve  $y'(x) = 3x + \frac{y}{2}$ ,  $y(0) = 1$  then find  $y(0.2)$  with  $n = 0.2$  using modified Euler's method. (06 Marks)
- b. Solve  $y(x) = 3e^x + 2y$ ,  $y(0) = 0$  then find  $y(0.1)$  with  $h = 0.1$  using Runge-Kutta method of fourth order. (07 Marks)
- c. Solve  $y'(x) = 2e^x - y$  and data is

x	0	0.1	0.2	0.3
y	2	2.010	2.040	2.090

Then find  $y(0.4)$  by using Adam's Bash forth method.

(07 Marks)

**Module-5**

- 9 a. By applying Milne's predictor and corrector method to compute  $y(0.4)$  give the differential equation  $\frac{d^2y}{dx^2} = 1 - \frac{dy}{dx}$  and the following table by initial value. (07 Marks)

x	0	0.1	0.2	0.3
y	1	1.1103	1.2427	1.3990
y'	1	1.2103	1.4427	1.6990

- b. Derive Euler's equation in the standard form  $\frac{\partial f}{\partial y} - \frac{d}{dx} \left( \frac{\partial f}{\partial y'} \right) = 0$ . (06 Marks)
- c. Find the extremal of the functional  $\int_{x_1}^{x_2} (y' + x^2 y'^2) dx$ . (07 Marks)

OR

- 10 a. By Runge Kutta method solve  $\frac{d^2y}{dx^2} = x \left( \frac{dy}{dx} \right)^2 - y^2$  for  $x = 0.2$  correct to four decimal places. Using initial condition  $y(0) = 1$ ,  $y'(0) = 0$ . (07 Marks)
- b. Prove that the shortest distance between two points in a plane is a straight line. (06 Marks)
- c. Find the curve on which the functional  $\int_0^1 [y'^2 + 12xy] dx$  with  $y(0) = 0$ ,  $y(1) = 1$ . (07 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18MATDIP31

## Third Semester B.E. Degree Examination, Aug./Sept.2020 Additional Mathematics - I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Prove that  $(1+i)^n + (1-i)^n = 2^{n/2+1} \cos \frac{n\pi}{4}$  (08 Marks)
- b. Express the complex number  $(2+3i) + \frac{1}{1-i}$  in the form  $a+ib$ . (06 Marks)
- c. Find the modulus and amplitude of the complex number  $1 - \cos\alpha + i \sin\alpha$ . (06 Marks)

OR

- 2 a. If  $\vec{A} = i+2j-3k$ ,  $\vec{B} = 3i-j+2k$  show that  $\vec{A}+\vec{B}$  is perpendicular to  $\vec{A}-\vec{B}$ . Also find the angle between  $2\vec{A}+3\vec{B}$  and  $\vec{A}+2\vec{B}$ . (08 Marks)
- b. Show that the vectors  $i-2j+3k$ ,  $2i+j+k$ ,  $3i+4j-k$  are coplanar. (06 Marks)
- c. Find the sine of the angle between  $\vec{A} = 4i-j+3k$  and  $\vec{B} = -2i+j-2k$ . (06 Marks)

### Module-2

- 3 a. Obtain the Maclaurin's series expansion of  $\sin x$  upto term containing  $x^4$ . (08 Marks)
- b. If  $u = \sin^{-1} \left[ \frac{x^2+y^2}{x-y} \right]$  prove that  $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \tan u$ . (06 Marks)
- c. If  $u = f(x-y, y-z, z-x)$  prove that  $\frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} = 0$ . (06 Marks)

OR

- 4 a. Prove that  $\log(1+x) = x - \frac{x^2}{2} + \frac{x^3}{3} - \frac{x^4}{4} + \dots$  by using Maclaurin's series. (08 Marks)
- b. If  $x = r \cos \theta$ ,  $y = r \sin \theta$  find  $\frac{\partial(x,y)}{\partial(r,\theta)}$ . (06 Marks)
- c. If  $z = e^{ax+by} f(ax-by)$  then show that  $b \frac{\partial z}{\partial x} + a \frac{\partial z}{\partial y} = 2abz$ . (06 Marks)

### Module-3

- 5 a. Find the angle between the surfaces  $x^2 + y^2 + z^2 = 9$  and  $z = x^2 + y^2 - 3$  at the point  $(2, -1, 2)$ . (08 Marks)
- b. Find the unit vector normal to the surface  $x^2y + 2xz = 4$  at  $(2, -2, 3)$ . (06 Marks)
- c. Show that the vector  $(-x^2 + yz)i + (4y - z^2x)j + (2xz - 4z)k$  is solenoidal. (06 Marks)

OR

- 6 a. A particle moves along the curve  $x = t^3 + 1$ ,  $y = t^2$ ,  $z = 2t + 3$  where  $t$  is the time. Find the components of its velocity and acceleration at  $t = 1$  in the direction  $\mathbf{i} + \mathbf{j} + 3\mathbf{k}$ . (08 Marks)
- b. Find the values of  $a$ ,  $b$ ,  $c$  such that  $\vec{F} = (x + y + az)\mathbf{i} + (bx + 2y - z)\mathbf{j} + (x + cy + 2z)\mathbf{k}$  is irrotational. (06 Marks)
- c. Find  $\text{div}\vec{F}$  and  $\text{curl}\vec{F}$  where  $\vec{F} = \nabla(x^3 + y^3 + z^3 - 3xyz)$ . (06 Marks)

Module-4

- 7 a. Obtain the reduction formula for  $\int_0^{\pi/2} \cos^n x \, dx$ ,  $n > 0$ . (08 Marks)
- b. Evaluate  $\int_0^1 \frac{x^9}{\sqrt{1-x^2}} \, dx$  (06 Marks)
- c. Evaluate  $\iint xy(x+y) \, dx \, dy$  over the area between  $y = x^2$  and  $y = x$ . (06 Marks)

OR

- 8 a. Obtain the reduction formula for  $\int_0^{\pi/2} \sin^n x \, dx$ ,  $n > 0$ . (08 Marks)
- b. Evaluate  $\int_0^{\infty} \frac{x^2}{(1-x^2)^{7/2}} \, dx$  (06 Marks)
- c. Evaluate  $\int_0^a \int_0^x \int_0^{x+y} e^{x+y+z} \, dz \, dy \, dx$  (06 Marks)

Module-5

- 9 a. Solve  $y(\log y)dx + (x - \log y)dy = 0$  (08 Marks)
- b. Solve  $x \frac{dy}{dx} + y = x^3 y^6$  (06 Marks)
- c. Solve  $(xy^2 - e^{1/x^3})dx - x^2 y \, dy = 0$  (06 Marks)

OR

- 10 a. Solve  $(5x^4 + 3x^2 y^2 - 2xy^3) \, dx + (2x^3 y - 3x^2 y^2 - 5y^4) \, dy = 0$  (08 Marks)
- b. Solve  $\frac{dy}{dx} + x \sin 2y = x^3 \cos^2 y$  (06 Marks)
- c. Solve  $(xy^3 + y)dx + 2(x^2 y^2 + x + y^4) \, dy = 0$  (06 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC32

**Third Semester B.E. Degree Examination, Aug./Sept. 2020**

## Network Theory

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Using source shifting and source transformation techniques, find the value of  $V_x$  for the circuit in Fig.Q1(a).

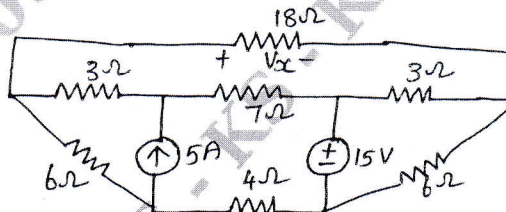


Fig.Q1(a)

(10 Marks)

- b. Use Mesh analysis to the circuit shown in Fig.Q1(b) to find the power supplied by 4V source.

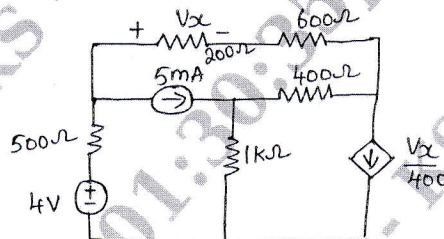


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Find the resistance  $R_{xy}$  for the circuit shown in Fig.Q2(a) using star-delta transformation.

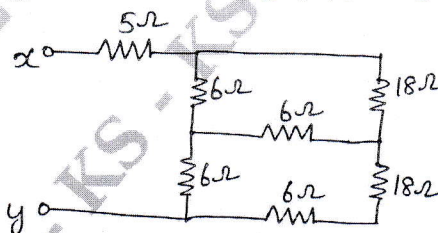


Fig.Q2(a)

(10 Marks)

- b. Find  $I_1$  in the circuit of Fig.Q2(b) using nodal analysis.

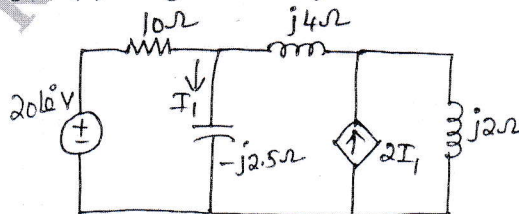


Fig.Q2(b)

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. Use superposition theorem to find  $i_0$  in the circuit shown in Fig.Q3(a).

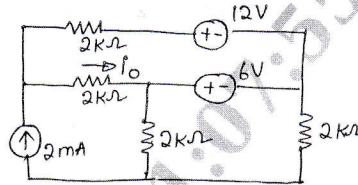


Fig.Q3(a)

(10 Marks)

- b. Find the Thevenin's and Norton's equivalent circuits at the terminals a-b for the circuit in Fig.Q3(b).

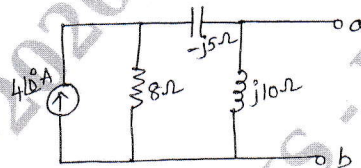


Fig.Q3(b)

(10 Marks)

**OR**

- 4 a. Find the current through  $(10 - j3)\Omega$  using Millman's theorem Refer Fig.Q4(a).

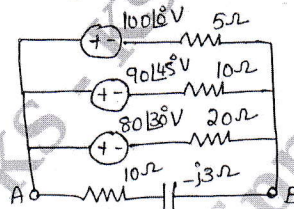


Fig.Q4(a)

(10 Marks)

- b. Find the value of  $R_L$  for the network shown in Fig.Q4(b) that results in maximum power transfer. Also find the value of maximum power.

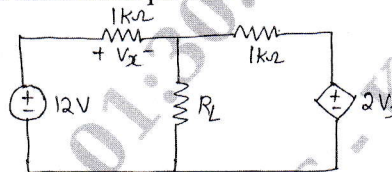


Fig.Q4(b)

(10 Marks)

**Module-3**

- 5 a. For the circuit shown in Fig.Q5(a), the switch K is changed from position 1 to position 2 at  $t = 0$ . Steady-state condition having been reached at position 1. Find the values of

$i, \frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$


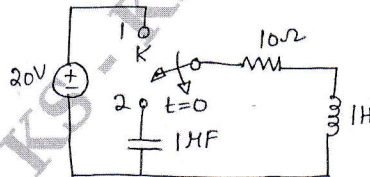


Fig.Q5(a)

(10 Marks)

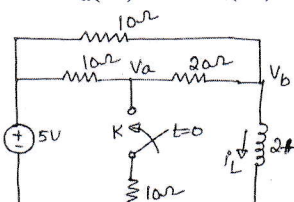- b. For the circuit shown in Fig.Q5(b), steady-state is reached with switch K open. At  $t = 0$ , the switch is closed. Determine the values  $V_a(0^-)$  and  $V_a(0^+)$ .



OR

- 6 a. In the network shown in Fig.Q6(a), the switch K is opened at  $t = 0$ . Find  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  at  $t = 0^+$ .

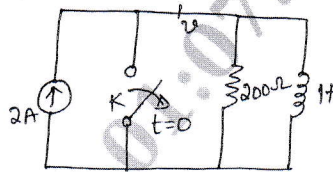


Fig.Q6(a)

(10 Marks)

- b. For the circuit shown in Fig.Q6(b) find :

- i)  $i(0^+)$  and  $v(0^+)$       ii)  $\frac{di(0^+)}{dt}$  and  $\frac{dv(0^+)}{dt}$       iii)  $i(\infty)$  and  $v(\infty)$ .

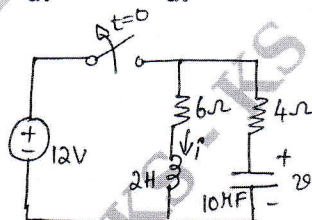


Fig.Q6(b)

(10 Marks)

**Module-4**

- 7 a. State and prove initial-value theorem and final-value theorem. (10 Marks)  
 b. For the circuit of Fig.Q7(b).  
 i) Write a differential equation for  $i_L(t)$     ii) find  $I_L(s)$     iii) solve for  $i_L(t)$ .

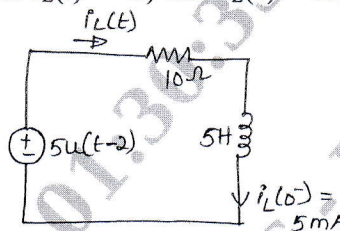


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Find the Laplace transform of the periodic signal  $x(t)$  shown in Fig.Q8(a).

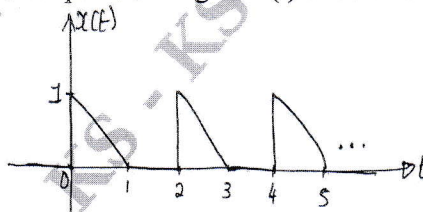


Fig.Q8(a)

(10 Marks)

- b. For the circuit shown in Fig.Q8(b), steady state is reached with the 100V source. At  $t = 0$ , switch k is opened. What is the current through the inductor at  $t = \frac{1}{2}$  seconds.

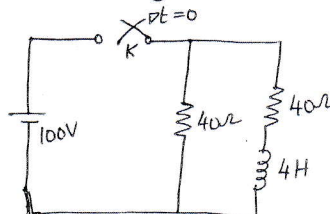


Fig.Q8(b)

(10 Marks)



**Module-5**

- 9 a. Explain h-parameters. Express h-parameters in terms of z-parameters.  
 b. Find y-parameters for the circuit shown in Fig.9(b).

(10 Marks)

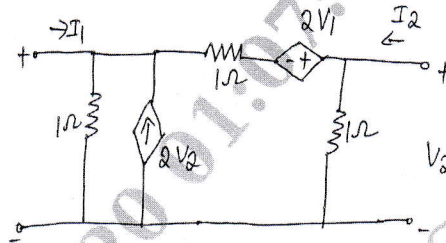


Fig. Q9(b)

(10 Marks)

**OR**

- 10 a. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.1\text{H}$  and  $C = 100\mu\text{F}$  and is connected across a 200V, variable frequency source, find :  
 i) Resonant frequency  
 ii) Impedance at this frequency  
 iii) Voltage drops across l and c at this frequency  
 iv) Quality factor  
 v) Bandwidth.  
 b. Find the value of  $R_1$  such that the circuit given in Fig.10(b) is resonant.

(07 Marks)

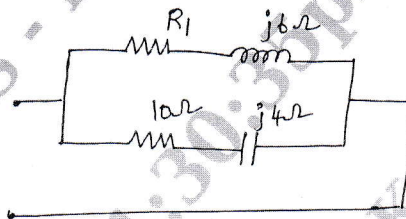


Fig.10(b)

(07 Marks)

- c. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01\text{H}$  and  $C = 0.01\mu\text{F}$  and it is connected across 10mV supply. Calculate :  
 i)  $f_0$  ii)  $Q_0$  iii) Bandwidth iv)  $f_1$  and  $f_2$  v)  $I_0$ .

(06 Marks)

\*\*\*\*\*



18EC33

**Module-5**

- 9 a. Explain thermal oxidation process with neat diagram. (10 Marks)  
b. What is metallization process explain with neat diagram by showing all the steps in the fabrication of p-n junctions. (10 Marks)

**OR**

- 10 a. Explain integration of other circuit elements with suitable diagrams. (10 Marks)  
b. Explain CMOS process of integration with the help of neat diagram. (10 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC34

## Third Semester B.E. Degree Examination, Aug./Sept.2020 Digital System Design

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Place the following equations into proper canonical forms:
  - i)  $f(abc) = a\bar{b} + a\bar{c} + bc$
  - ii)  $f(abcd) = (a + \bar{b})(a + \bar{b} + d)$  (06 Marks)
- b. Identify all the prime implicants and essential prime implicants of the Boolean function using K-map.  
 $f(abcd) = \Sigma(0, 1, 2, 5, 6, 7, 8, 9, 10, 13, 14, 15)$  (06 Marks)
- c. Find the minimal sum and minimal product for the function using K-map.  
 $f(abcd) = \Sigma(6, 7, 9, 10, 13) + \Sigma d(1, 4, 5, 11, 15)$  (08 Marks)

OR

- 2 a. Represent the number of days in a month for a non-leap year by a truth table, indicating the output of invalid input if any by '0'. (05 Marks)
- b. Find all the prime implicants of the function using Quine-McClusky method.  
 $f(abcd) = \Sigma(7, 9, 12, 13, 14, 15) + d(4, 11)$  (10 Marks)
- c. Simplify the given Boolean equation using K-map:  
 $f(abcd) = \pi(1, 2, 3, 4, 9, 10) + \pi d(0, 14, 15)$  (05 Marks)

### Module-2

- 3 a. Implement full subtractor using 74138 decoder. (06 Marks)
- b. Design 2-bit magnitude comparator. (08 Marks)
- c. Implement Boolean function using 8:1 MUX treat a, b, c as select lines:  
 $f(abcd) = \Sigma(0, 1, 5, 6, 7, 9, 10, 15)$  (06 Marks)

OR

- 4 a. Implement the Boolean function  $f(abcd) = \Sigma(0, 2, 4, 5, 7, 9, 10, 14)$  using multiplexers with two 4:1 MUX with variable a, d connected to their select lines in the first level and one 2:1 MUX with variable 'C' connected to its select lines in the second level. (10 Marks)
- b. Implement Boolean function  $f(abcd) = \Sigma(4, 5, 7, 8, 10, 12, 15)$  using 4:1 MUX and external gates:
  - (i) a, b are connected to select line  $a_1 a_0$  respectively
  - (ii) c, d are connected to select lines  $a_1 a_0$  respectively. (10 Marks)

### Module-3

- 5 a. Explain the operation of switch debouncer using SR latch with the help of circuit and waveforms. (07 Marks)
- b. Explain Master Slave JK F/F with the help of circuit diagram and waveforms. (07 Marks)
- c. Design a 4-bit binary ripple-up counter using negative edge triggered JK flip-flop. (06 Marks)

OR

- 6 a. Explain positive edge triggered D-flip-flop with the help of circuit diagram and waveforms. (08 Marks)
- b. Design a 4-bit universal shift register using positive edge triggered D-flip-flop and multiplexers to operate as indicated below:
- | Mode select | Operation     |
|-------------|---------------|
| 00          | Hold          |
| 01          | Right shift   |
| 10          | Left shift    |
| 11          | Parallel load |
- (08 Marks)
- c. Write the difference between ripple counter and synchronous counter. (04 Marks)

**Module-4**

- 7 a. Design 3 bit synchronous up-counter using J-K flip-flop. (10 Marks)
- b. Design a mod-6 synchronous counter using D-flip flop for the sequence 0-2-3-6-5-1. (10 Marks)

OR

- 8 a. Draw and explain block diagram of Moore model and mealy model. (06 Marks)
- b. Design a synchronous circuit using positive edge triggered J-K flip-flop with minimal combinational gating to generate the sequence:  
 0 – 1 – 2 – 0 if input x = 0  
 0 – 2 – 1 – 0 if input x = 1  
 Provide an output which goes high to indicate the non-zero state in the sequence 0 – 1 – 2 – 0. (08 Marks)
- c. Design mod-5 synchronous counter using TF/F. (06 Marks)

**Module-5**

- 9 a. A sequential circuit has one input (x) and one output (z) the circuit examines groups of four consecutive inputs and produces an output z = 1 if the input sequence 0101 or 1001 occurs. The circuit resets after every four inputs. Find the mealy state graph typical sequence is 0101 0010 1001 0100. (10 Marks)
- b. Explain with block diagram design and serial Adder with accumulator. (10 Marks)

OR

- 10 a. Write a short note on 4 × 4 bit binary parallel multiplication. (10 Marks)
- b. List the guide lines for construction of state graphs. (10 Marks)

\* \* \* \* \*



--	--	--	--	--	--	--	--	--	--

## Third Semester B.E. Degree Examination, Aug./Sept.2020 Power Electronics and Instrumentation

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Define power electronics. Mention the different power electronic circuits. (04 Marks)
- b. With the help of the static V-I characteristics, explain the three modes of operation of the SCR. (10 Marks)
- c. Explain class-B commutation with necessary circuit diagram and waveforms. (06 Marks)

OR

- 2 a. Define commutation. Differentiate between natural and forced commutation. (06 Marks)
- b. Explain the gate characteristics of the SCR. (04 Marks)
- c. Explain the working of a UJT firing circuit for a full wave rectifier using SCR with necessary circuit diagram and waveforms. (10 Marks)

### Module-2

- 3 a. Differentiate between uncontrolled and controlled rectifier. (04 Marks)
- b. Explain the operation of single-phase full converter with resistive load with necessary circuit diagram and waveforms. Derive the expression for the average and rms output voltage. (10 Marks)
- c. Explain the operation of step-up chopper. (06 Marks)

OR

- 4 a. With necessary circuit diagram and waveforms, explain the working of single phase half wave converter with inductive load. (10 Marks)
- b. Explain the working of step-down chopper. (06 Marks)
- c. Explain the effect of freewheeling diode. (04 Marks)

### Module-3

- 5 a. Explain the working of single phase full bridge inverter with necessary circuit diagram and waveforms. (08 Marks)
- b. Define the following terms as applied to an electronic instrument:
  - i) Accuracy
  - ii) Precision
  - iii) Resolution(06 Marks)
- c. Sketch and explain the operation of a multirange ammeter. (06 Marks)

OR

- 6 a. Explain the working of isolated forward SMPS with necessary circuit diagram. (08 Marks)
- b. Calculate series connected multiplier resistance with D'Arsonal movement with an internal resistance of  $50\Omega$  and full scale deflection current of  $2\text{mA}$  when converted into a multirange d.c. voltmeter with ranges from  $0-20\text{V}$ ,  $0-40\text{V}$ ,  $0-150\text{V}$  and  $0-200\text{V}$ . (08 Marks)
- c. Briefly explain the Gross error and absolute error with an example. (04 Marks)

**Module-4**

- 7 a. Discuss the operation of dual slope integrating type DVM with the help of block diagram. (08 Marks)
- b. Explain an unbalanced Wheatstone bridge circuit. Determine the amount of deflection due to unbalance of Wheatstone bridge. (08 Marks)
- c. An inductance comparison bridge is used to measure inductive impedance at a frequency of 5Hz. The bridge constants at balance are  $L_3 = 10\text{mH}$ ,  $R_1 = 10\text{K}\Omega$ ,  $R_2 = 40\text{K}\Omega$ ,  $R_3 = 100\text{K}\Omega$ . Find the equivalent series circuit of an unknown impedance. (04 Marks)

**OR**

- 8 a. Explain the working of a digital frequency meter with the help of a block diagram. (10 Marks)
- b. Explain the operation of the Wein's bridge with a neat circuit diagram. Derive an expression for the frequency. (07 Marks)
- c. If the three arms of a Wheatstone's bridge have the resistances  $R_1 = 2\text{K}\Omega$ ,  $R_2 = 10\text{K}\Omega$  and  $R_3 = 40\text{K}\Omega$ . Find the unknown resistance. (03 Marks)

**Module-5**

- 9 a. Explain the construction, working principle and operation of LVDT. Show the characteristics curve. (10 Marks)
- b. Mention the advantages and limitations of thermistor. (04 Marks)
- c. Briefly explain the analog weight scale. (06 Marks)

**OR**

- 10 a. Explain the structure and operation of programmable logic controller. (07 Marks)
- b. Explain the operation of resistive position transducer. (05 Marks)
- c. Derive an expression for the gauge factor of bonded resistance wire strain gauge. (08 Marks)

\* \* \* \* \*