

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18MAT31

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Transform Calculus, Fourier Series and Numerical Techniques

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Evaluate (i) $L\left\{\frac{\cos 2t - \cos 3t}{t}\right\}$ (ii) $L(t^2 e^{-3t} \sin 2t)$ (06 Marks)
- b. If $f(t) = \begin{cases} t, & 0 \leq t \leq a \\ 2a - t, & a \leq t \leq 2a \end{cases}$, $f(t + 2a) = f(t)$ then show that $L(f(t)) = \frac{1}{s^2} \tanh\left(\frac{as}{2}\right)$ (07 Marks)
- c. Solve by using Laplace Transforms
 $\frac{d^2y}{dt^2} + 4\frac{dy}{dt} + 4y = e^{-t}$, $y(0) = 0$, $y'(0) = 0$ (07 Marks)

OR

- 2 a. Evaluate $L^{-1}\left(\frac{4s+5}{(s+1)^2(s+2)}\right)$ (06 Marks)
- b. Find $L^{-1}\left(\frac{s}{(s^2+a^2)^2}\right)$ by using convolution theorem. (07 Marks)
- c. Express $f(t) = \begin{cases} \sin t, & 0 \leq t < \pi \\ \sin 2t, & \pi \leq t < 2\pi \\ \sin 3t, & t \geq 2\pi \end{cases}$
 in terms of unit step function and hence find its Laplace Transform. (07 Marks)

Module-2

- 3 a. Obtain fourier series for the function $f(x) = |x|$ in $(-\pi, \pi)$ (06 Marks)
- b. Expand $f(x) = \frac{(\pi-x)^2}{4}$ as a Fourier series in the interval $(0, 2\pi)$ and hence deduce that
 $\frac{\pi^2}{12} = \frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \frac{1}{4^2} + \dots$ (07 Marks)
- c. Express y as a Fourier series upto the second harmonic given :

x:	0	60	120	180	240	300
y:	4	3	2	4	5	6

(07 Marks)

OR

- 4 a. Find the Half-Range sine series of $\pi x - x^2$ in the interval $(0, \pi)$ (06 Marks)
- b. Obtain fourier expansion of the function $f(x) = 2x - x^2$ in the interval $(0, 3)$. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

- c. Obtain the Fourier expansion of y upto the first harmonic given :

x	0	1	2	3	4	5
y	9	18	24	28	26	20

(07 Marks)

Module-3

- 5 a. If $f(x) = \begin{cases} 1, & |x| < a \\ 0, & |x| > a \end{cases}$, find the Fourier transform of $f(x)$ and hence find the value of $\int_0^{\infty} \frac{\sin x}{x} dx$ (06 Marks)
- b. Find the infinite Fourier cosine transform of $e^{-\alpha x}$. (07 Marks)
- c. Solve using z-transform $y_{n+2} - 4y_n = 0$ given that $y_0 = 0, y_1 = 2$ (07 Marks)

OR

- 6 a. Find the fourier sine transform of $f(x) = e^{-|x|}$ and hence evaluate $\int_0^{\infty} \frac{x \sin mx}{1+x^2} dx$; $m > 0$. (06 Marks)
- b. Obtain the z-transform of $\cos n\theta$ and $\sin n\theta$. (07 Marks)
- c. Find the inverse z-transform of $\frac{4z^2 - 2z}{z^3 - 5z^2 + 8z - 4}$ (07 Marks)

Module-4

- 7 a. Solve $\frac{dy}{dx} = x^3 + y$, $y(1) = 1$ using Taylor's series method considering up to fourth degree terms and find $y(1.1)$. (06 Marks)
- b. Given $\frac{dy}{dx} = 3x + \frac{y}{2}$, $y(0) = 1$ compute $y(0.2)$ by taking $h = 0.2$ using Runge - Kutta method of fourth order. (07 Marks)
- c. If $\frac{dy}{dx} = 2e^x - y$, $y(0) = 2$, $y(0.1) = 2.010$, $y(0.2) = 2.040$ and $y(0.3) = 2.090$, find $y(0.4)$ correct to 4 decimal places using Adams-Bashforth method. (07 Marks)

OR

- 8 a. Use fourth order Runge-Kutta method, to find $y(0.8)$ with $h = 0.4$, given $\frac{dy}{dx} = \sqrt{x+y}$, $y(0.4) = 0.41$ (06 Marks)
- b. Use modified Euler's method to compute $y(20.2)$ and $y(20.4)$ given that $\frac{dy}{dx} = \log_{10} \left(\frac{x}{y} \right)$ with $y(20) = 5$ Taking $h = 0.2$. (07 Marks)
- c. Apply Milne's predictor-corrector formulae to compute $y(2.0)$ given $\frac{dy}{dx} = \frac{x+y}{2}$ with

x	0.0	0.5	1.0	1.5
y	2.000	2.6360	3.5950	4.9680

(07 Marks)

Module-5

- 9 a. Using Runge-Kutta method, solve

$$\frac{d^2y}{dx^2} = x \left(\frac{dy}{dx} \right)^2 - y^2, \text{ for } x = 0.2, \text{ correct to four decimal places, using initial conditions}$$

$$y(0) = 1, y'(0) = 0$$

(07 Marks)

- b. Derive Euler's equation in the standard form viz, $\frac{\partial f}{\partial y} - \frac{d}{dx} \left(\frac{\partial f}{\partial y'} \right) = 0$ (07 Marks)

- c. Find the extremal of the functional $\int_{x_1}^{x_2} (y^2 + y'^2 + 2ye^x) dx$ (06 Marks)

OR

- 10 a. Given the differential equation $2 \frac{d^2y}{dx^2} = 4x + \frac{dy}{dx}$ and the following table of initial values:

x	1	1.1	1.2	1.3
y	2	2.2156	2.4649	2.7514
y'	2	2.3178	2.6725	2.0657

Compute $y(1.4)$ by applying Milne's Predictor-corrector formula. (07 Marks)

- b. Prove that geodesics of a plane surface are straight lines. (07 Marks)

- c. On what curves can the functional $\int_0^1 (y'^2 + 12xy) dx$ with $y(0) = 0, y(1) = 1$ can be

extremized? (06 Marks)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18MATDIP31

Third Semester B.E. Degree Examination, Feb./Mar. 2022

Additional Mathematics – I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Find the modulus and amplitude of the complex number : $\frac{(2-3i)(2+i)^2}{1+i}$. (07 Marks)
- b. Prove that $\left(\frac{1+\cos\theta+i\sin\theta}{1+\cos\theta-i\sin\theta}\right)^n = \cos n\theta + i\sin n\theta$. (06 Marks)
- c. Show that the vectors $\vec{a}-2\vec{b}+3\vec{c}$, $-2\vec{a}+3\vec{b}-4\vec{c}$, $-\vec{b}+2\vec{c}$ are coplanar. (07 Marks)

OR

- 2 a. Given $\vec{a} = 2\hat{i} + 2\hat{j} - \hat{k}$, $\vec{b} = 6\hat{i} - 3\hat{j} + 2\hat{k}$. Find : i) $\vec{a} \cdot \vec{b}$ ii) $\vec{a} \times \vec{b}$ iii) $|\vec{a} \times \vec{b}|$. (07 Marks)
- b. Determine the value of λ , so that $\vec{a} = 2\hat{i} + \lambda\hat{j} - \hat{k}$, and $\vec{b} = 4\hat{i} - 2\hat{j} - 2\hat{k}$, are perpendicular. (06 Marks)
- c. Express $1 - i\sqrt{3}$ in the polar form and hence find its modulus and amplitude. (07 Marks)

Module-2

- 3 a. Using Euler's theorem, prove that $xu_x + yu_y = -3\cot u$ where $u = \sin^{-1}\left(\frac{x^2y^2}{x+y}\right)$. (07 Marks)
- b. Using Maclaurin's series, prove that $\sqrt{1+\sin 2x} = 1 + x - \frac{x^2}{2} - \frac{x^3}{3} + \frac{x^4}{24} + \dots$. (06 Marks)
- c. If $u = x + 3y^2$, $v = 4x^2yz$, $w = 2z^2 - xy$, evaluate $\frac{\partial(u,v,w)}{\partial(x,y,z)}$ at the point $(1, -1, 0)$. (07 Marks)

OR

- 4 a. Obtain Maclaurin's series expansion for the function e^x upto x^4 . (07 Marks)
- b. If $u = \sin^{-1}\left(\frac{x^3 + y^3}{x+y}\right)$ prove that $x\frac{\partial u}{\partial x} + y\frac{\partial u}{\partial y} = 2 \tan u$. (06 Marks)
- c. If $u = f\left(\frac{x}{y}, \frac{y}{z}, \frac{z}{x}\right)$, prove that $x\frac{\partial u}{\partial x} + y\frac{\partial u}{\partial y} + z\frac{\partial u}{\partial z} = 0$. (07 Marks)

Module-3

- 5 a. A particle moves along the curve $x = (1-t^3)$, $y = (1+t^2)$, $z = (2t-5)$ determine its velocity and acceleration at $t = 1$ sec. (07 Marks)
- b. If $\vec{F} = 2x^2\hat{i} - 3yz\hat{j} + xz^2\hat{k}$, and $\phi = 2z - x^3y$, find $\vec{F} \cdot (\nabla\phi)$ and $\vec{F} \times (\nabla\phi)$ at $(1, -1, 1)$. (06 Marks)
- c. Find the constants a, b, c so that $\vec{f} = (x+2y+az)\hat{i} + (bx-3y-z)\hat{j} + (4x+cy+2z)\hat{k}$ is irrotational. (07 Marks)

OR

- 6 a. Find the directional derivative of $\phi = x^2yz + 4xz^2$ at $(1, -2, -1)$ along $\vec{a} = 2\hat{i} - \hat{j} - 2\hat{k}$ (07 Marks)
- b. Find curl \vec{f} given that $\vec{f} = xyz^2\hat{i} + xy^2z\hat{j} + x^2yz\hat{k}$. (06 Marks)
- c. If $\vec{f} = x^2\hat{i} + y^2\hat{j} + z^2\hat{k}$ and $\vec{g} = yz\hat{i} + zx\hat{j} + xy\hat{k}$. Show that $\vec{f} \times \vec{g}$ is a solenoidal vector. (07 Marks)

Module-4

- 7 a. Obtain the reduction formula, $I_n = \int \cos^n x dx$, where n is a positive integer. (07 Marks)
- b. Evaluate $\int_0^1 \int_x^{\sqrt{x}} xy dy dx$. (06 Marks)
- c. Evaluate $\int_0^1 \int_0^1 \int_0^1 (x + y + z) dx dy dz$. (07 Marks)

OR

- 8 a. Evaluate : $\int_0^{\pi/6} \sin^6(3x) dx$. (07 Marks)
- b. Evaluate : $\int_0^{\pi} x \sin^4 x \cos^6 x dx$. (06 Marks)
- c. Evaluate $\int_0^1 \int_0^1 \int_0^y xyz dx dy dz$. (07 Marks)

Module-5

- 9 a. Solve : $(2x + y + 1) dx + (x + 2y + 1) dy = 0$. (07 Marks)
- b. Solve : $(4xy + 3y^2 - x) dx + (x^2 + 2xy) dy = 0$. (06 Marks)
- c. Solve : $y(2xy + e^x) dx - e^x dy = 0$. (07 Marks)

OR

- 10 a. Solve : $(5x^4 + 3x^2y^2 - 2xy^3) dx + (2x^3y - 3x^2y^2 - 5y^4) dy = 0$. (07 Marks)
- b. Solve : $y(2xy + 1) dx - x dy = 0$. (06 Marks)
- c. Solve : $\frac{dy}{dx} + y \cot x = \cos x$. (07 Marks)

CBCGS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC32

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Network Theory

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Determine current through 12Ω resistor shown in Fig.Q1(a), using source transformation.

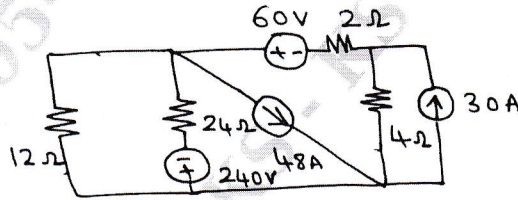


Fig.Q1(a)

(08 Marks)

- b. Find the equivalent resistance of the circuit shown in Fig.Q1(b), using star delta transformation.

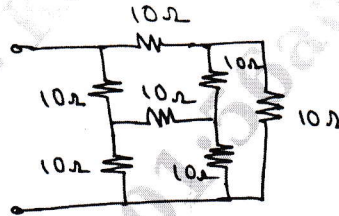


Fig.Q1(b)

(08 Marks)

- c. Discuss the dependent sources.

(04 Marks)

OR

- 2 a. Using loop analysis, find the current through 10Ω resistor for the circuit shown in Fig.Q2(a).

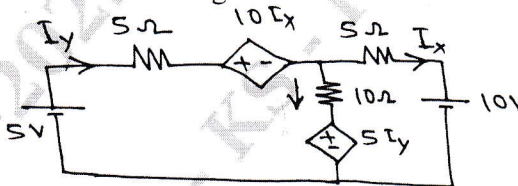


Fig.Q2(a)

(08 Marks)

- b. For the network shown in Fig.Q2(b), determine node voltages V_1, V_2, V_3 and V_4 using nodal analysis.

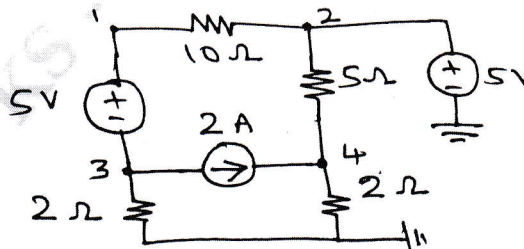


Fig.Q2(b)

(08 Marks)

- c. Explain the super Mesh with example.

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg, $42+8=50$, will be treated as malpractice.

Module-2

- 3 a. Using super position theorem, find the current through 20Ω resistor shown in Fig.Q3(a).

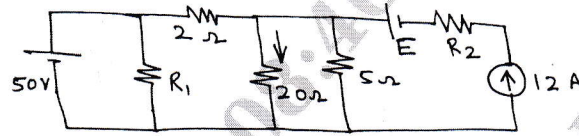


Fig.Q3(a)

(08 Marks)

- b. Using Millman's theorem, determine the current through $(2 + j2)\Omega$ impedance for the network shown in Fig.Q3(b).

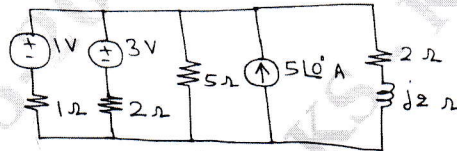


Fig.Q3(b)

(08 Marks)

- c. State the Norton's theorem and also write the procedure to be followed for solving the problem.

(04 Marks)

OR

- 4 a. What should be the value of R such that maximum power transfer can take place from the rest of the network to R . Obtain the amount of this power for circuit shown in Fig.Q4(a).

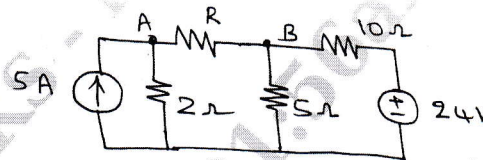


Fig.Q4(a)

(08 Marks)

- b. Obtain the Thevenin's equivalent circuit across AB for the circuit shown in Fig.Q4(b).

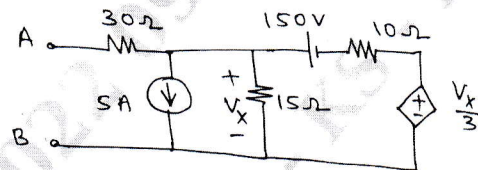


Fig.Q4(b)

(08 Marks)

- c. State the maximum power transfer theorem and also write equation of P_{max} for both DC and AC circuits.

(04 Marks)

Module-3

- 5 a. Explain the transient behavior of the resistance, inductance and capacitor. Also write the procedure for evaluating transient behavior.

(10 Marks)

- b. In the network shown in Fig.Q5(b), a steady state is reached with the switch 'K' open. At $t = 0$ the switch is closed. Determine the value of $V_a(0^+)$ and $V_a(0^-)$.

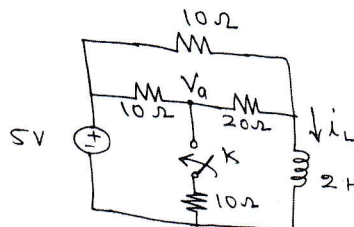


Fig.Q5(b)

(10 Marks)

OR

- 6 a. For the network shown in Fig.Q6(a) $V_1(t) = e^{-t}$ for $t \geq 0$ and is zero for all $t < 0$. If the capacitor is initially uncharged determine the value of $\frac{d^2 V_2}{dt^2}$ and $\frac{d^3 V_2}{dt^3}$ at $t = 0$.

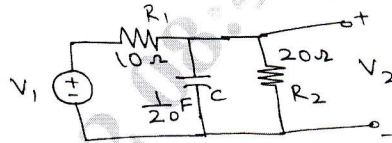


Fig.Q6(a)

(10 Marks)

- b. The switch 'S' is changed from position 1 to position 2 at $t = 0$. Steady state conditions have been reached in position 1. Find the value of i , $\frac{di}{dt}$ and $\frac{d^2 i}{dt^2}$ at $t = 0^+$ for the circuit shown in Fig.Q6(b).

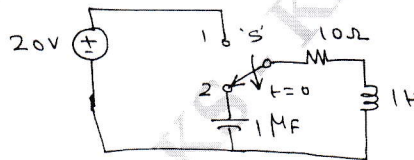


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. Find the Laplace transform of $f(t)$ shown in Fig.Q7(a).

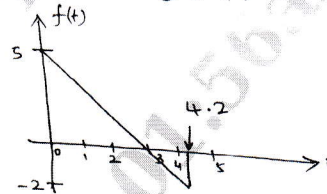


Fig.Q7(a)

(10 Marks)

- b. Find the Laplace transform of the pulse shown in Fig.Q7(b).

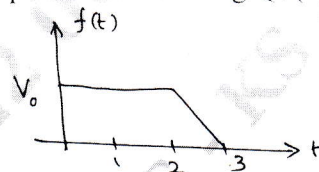


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Find $i(t)$ for the circuit shown in Fig.Q8(a).

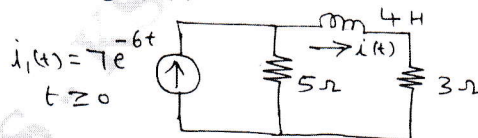


Fig.Q8(a)

(10 Marks)

- b. A voltage pulse of 10V and 5μsec duration is applied to the RC network shown in Fig.Q8(b). Find the current $i(t)$.

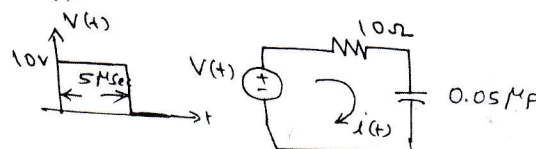


Fig.Q8 (b)

(10 Marks)

Module-5

- 9 a. Obtain y-parameters in terms of z-parameters and h-parameters. (10 Marks)
 b. For the network shown in Fig.Q9(b), find the T-parameters.

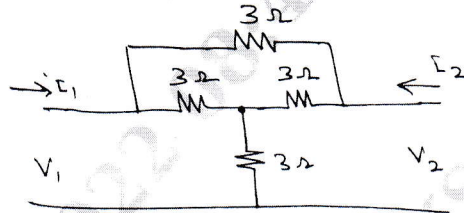


Fig.Q9(b)

(10 Marks)

OR

- 10 a. Derive the expression of bandwidth, half power frequencies and selectivity of a series resonance circuit. (10 Marks)
 b. For the parallel resonant circuit shown in Fig.Q10(b), find I_0 , I_L , I_C , f_0 and dynamic resistance.

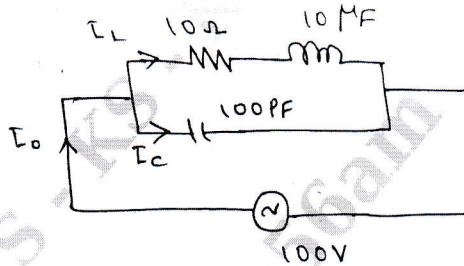


Fig.Q10(b)

(10 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC33

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Electronic Devices

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Explain classification of semiconductor insulator and metals using energy band diagram. (08 Marks)
 - Explain different types of bonding forces in solids. (04 Marks)
 - What are intrinsic and extrinsic materials? Explain briefly by taking suitable example. (08 Marks)

OR

- Define Hall effect in semiconductor. Obtain an expression for mobility in terms of Hall coefficient and resistivity. (08 Marks)
 - Consider a semiconductor bar with width $w = 0.1$ mm, thickness $t = 10$ μm , length $L = 5$ mm. For $B = 10$ KG (1 KG = 10^{-5} wb/cm²) and current of 1 mA. We have $V_{AB} = -2$ mV and $V_{CD} = 100$ mV. Find the type, concentration and mobility of the majority carrier. [Refer Fig.Q2(b)]

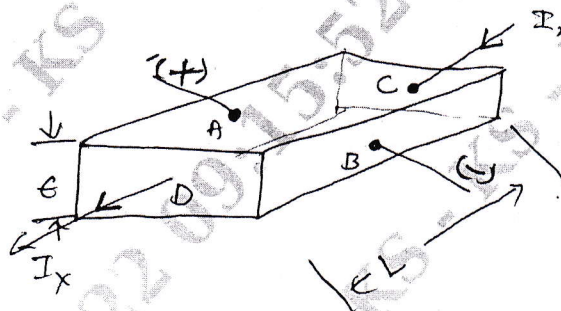


Fig.Q2(b)

- Derive an expression for conductivity and mobility from random thermal motion or electron in solid. (08 Marks)

Module-2

- Explain the reverse bias p-n junction indicating the minority carrier distribution and variation of quasi fermi levels. (10 Marks)
 - With a neat diagram, explain in detail Avalanche Breakdown and derive an approximate analysis of avalanche multiplication. (10 Marks)

OR

- Derive an expression for current and voltage for an illuminated junction of photodiode and discuss the operation in various quadrants in I-V characteristic. (08 Marks)
 - Explain the structure and operation of solar cell. Indicate the significance of Fill Factor. (08 Marks)
 - A solar cell has a short circuit current of 100 mA and open circuit voltage of 0.8 V under full solar illumination fill factor is 0.7. What is maximum power delivered to load by this cell? (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Explain the summary of hole flow and electron flow in p-n-p transistor with proper biasing and list three dominant mechanism which accounts for I_B . (10 Marks)
 b. Explain the process flow for double polysilicon self aligned BJT Fabrication. (10 Marks)

OR

- 6 a. Derive Eber's mott modes for Assymetric Transistor (coupled diode model). (10 Marks)
 b. Write short notes on: (i) Base narrowing (ii) Avalanche Breakdown in transistor (10 Marks)

Module-4

- 7 a. Explain the structure and operation of pn JFET by varying V_{GS} and V_{DS} independently. (06 Marks)
 b. Write the small signal equivalent circuit of JFET and obtain the expression for transconductance (g_m) and plot the graph with respect to V_{gs} . (06 Marks)
 c. Explain the operation of MOS capacitor using energy band diagram for p-type substrate when:
 (i) Negative gate bias
 (ii) Moderate positive gate bias
 (iii) Large positive gate bias (08 Marks)

OR

- 8 a. Explain the ideal capacitance voltage characteristics of an MOS capacitor with p-type substrate. (08 Marks)
 b. Explain the operation of n-channel enhancement MOSFET and obtain the current voltage relationship. (08 Marks)
 c. Write the different types of MOS structures and symbols for each. (04 Marks)

Module-5

- 9 Explain briefly the various steps involved in the fabrication of p-n junction:
 a. Rapid thermal processing (05 Marks)
 b. Ion implementation (05 Marks)
 c. Chemical Vapor Deposition (CVD) (05 Marks)
 d. Photolithography (05 Marks)

OR

- 10 a. Write a note on Integrated Circuit (IC) and its advantages and types of ICs. (10 Marks)
 b. Explain the fabrication of CMOS twin well process. (10 Marks)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC34

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Digital System Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define and explain the combinational logic circuit along with block diagram. (06 Marks)
- b. Develop the canonical minterm and maxterm forms in decimal notation for the following Boolean functions:
 - i) $X = f(a, b, c, d) = \bar{a}b + c\bar{d}$
 - ii) $Y = f(a, b, c) = (\bar{a} + b)(b + \bar{c})$ (08 Marks)
- c. Simplify the following function using K-map method and also construct logic circuit for the simplified equation (function). (06 Marks)
 $Y = f(a, b, c, d) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 14).$

OR

- 2 a. Simplify the following Boolean function by using Q-M method:
 $X = f(a, b, c) = \sum(0, 1, 2, 3, 4, 5, 6).$ (10 Marks)
- b. Design a combinational logic circuit for valid single digit BCD data, the output is 1 whenever a number is greater than 5 appears at the input. (05 Marks)
- c. Identify the PI and EPI for the following function: (05 Marks)
 $M = f(a, b, c, d) = \sum(1, 2, 3, 5, 7, 11, 12, 13, 14, 15).$

Module-2

- 3 a. Draw and explain the circuit for 3 to 8 decoder. (06 Marks)
- b. Design and implement a full adder circuit using logic gates. (08 Marks)
- c. Write a short notes on PLD's and FPGA. (06 Marks)

OR

- 4 a. Define MUX and explain 4:1 MUX with the help of logic diagram using gates. (06 Marks)
- b. Explain 4-bit carry look-ahead adder with diagram. (08 Marks)
- c. Design and implement 1-bit comparator circuit. (06 Marks)

Module-3

- 5 a. Compare sequential circuit and combinational circuits. (06 Marks)
- b. Write a short notes on SR-latch. (06 Marks)
- c. Illustrate master-slave J-K flip-flop using NAND Gates. (08 Marks)

OR

- 6 a. Distinguish between synchronous and asynchronous counter. (06 Marks)
- b. Explain 4-bit universal shift register along with diagram. (08 Marks)
- c. Explain the working of clocked SR-FF using NAND Gates. (06 Marks)

Module-4

- 7 a. Explain Mealy and Moore model with diagrams. (10 Marks)
 b. Design and develop Mod-6 synchronous counter using T-FF. (10 Marks)

OR

- 8 a. Construct the excitation table, transition table, state table and state diagram for the following sequential circuit. (Refer Fig.Q.8(a)). (14 Marks)

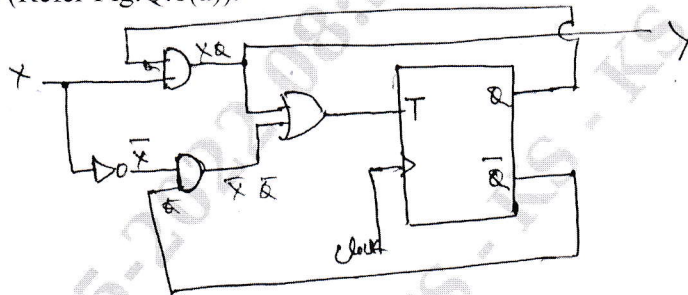


Fig.Q.8(a)

- b. List out the applications of shift registers along with brief explanation. (06 Marks)

Module-5

- 9 a. Explain the operation of serial adder with accumulator. (12 Marks)
 b. Illustrate state assignment rules. (08 Marks)

OR

- 10 a. Write a short notes on:
 i) Sequential circuit design steps (10 Marks)
 ii) BCD to Ex-3 code convertor. (10 Marks)
 b. Explain 4-bit Ring and Johnson counter along with diagram. (10 Marks)

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC35

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Computer Organization and Architecture

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the basic operational concept between the processor and memory with neat block diagram. (08 Marks)
- b. Explain the various parameters affecting the performance of a computer and also provide the basic performance equation. (08 Marks)
- c. Write a short note on single bus structure with neat diagram. (04 Marks)

OR

- 2 a. List out and explain the three systems used for representing signed numbers and also brief about the modular number system concept. (08 Marks)
- b. Explain IEEE standard used for single and double precision floating point number representation with examples. (08 Marks)
- c. Write a short note on Big-endian and little-endian assignment. (04 Marks)

Module-2

- 3 a. What is addressing mode? Explain any four addressing modes with examples. (08 Marks)
- b. What are assembler directives? Explain about the various directives used in the program with example. (08 Marks)
- c. Write a short note on the assembly and execution of programs. (04 Marks)

OR

- 4 a. With neat diagram and program example, explain a simple I/O task between processor, keyboard and display. (10 Marks)
- b. What is subroutine? Illustrate the subroutine function with parameter passing by value and reference with suitable program. (10 Marks)

Module-3

- 5 a. Explain the concept of memory mapped I/O with neat diagram of I/O interface with program example. (10 Marks)
- b. Write short notes on: (i) Interrupt hardware (ii) Interrupt nesting (10 Marks)

OR

- 6 a. What is an interrupt? Explain about various implementation techniques of interrupt. (10 Marks)
- b. Explain how simultaneous interrupt request is handled using the concept of Daisy Chain. (10 Marks)

Module-4

- 7 a. Explain the internal organization of memory chips with example. (08 Marks)
- b. Explain the internal organization of $2M \times 8$ DRAM chip with neat diagram. (08 Marks)
- c. Write a short note on ROM. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 8 a. Discuss about the use of cache memory in the processor system. (08 Marks)
- b. What is virtual memory? Explain its organization with neat diagram. (08 Marks)
- c. Write a short note on magnetic hard disk. (04 Marks)

Module-5

- 9 a. Explain single-bus organization of the data path inside a processor with neat diagram. (10 Marks)
- b. Explain the process of fetching a data word from memory using respective registers of a processor with neat diagram. (10 Marks)

OR

- 10 a. Explain the control signal generation required for proper sequence of instructions in the processor. (10 Marks)
- b. What is microprogrammed control? Explain its basic organization with suitable diagram and example. (10 Marks)

* * * * *

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC36

Third Semester B.E. Degree Examination, Feb./Mar. 2022 Power Electronics and Instrumentation

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Mention the different types of power electronic converters. Explain the significance, functions and applications of them. (07 Marks)
 - Explain the static Anode-Cathode characteristics of SCR with circuit diagram and V-I characteristics. (08 Marks)
 - Explain the basic operation of the unijunction transistor with basic UJT structure, UJT symbol and equivalent circuit. (05 Marks)

OR

- Mention the applications of power electronics in various sectors. (07 Marks)
 - The latching current of a thyristor circuit is 50mA. The duration of the firing pulse is 50 μ s. Will the thyristor get fired? (05 Marks)

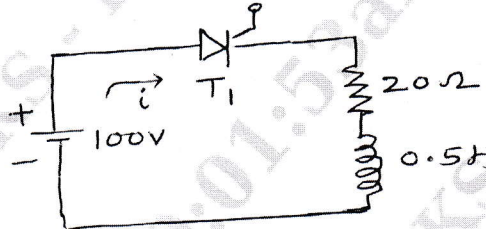


Fig.Q.2(b)

- Explain the operation of the resistance firing circuit with associated voltage waveforms. Derive the relevant expressions. (08 Marks)

Module-2

- Explain the operation of the single phase half wave controlled rectifier with resistive load using circuit and waveforms. (10 Marks)
 - Give basic chopper classification with different chopper configurations. (05 Marks)
 - A dc chopper circuit connected to a 100V dc source supplies an inductive load having 40mH in series with a resistance of 5 Ω . A freewheeling diode is placed across the load. The load current varies between the limits of 10A and 12A. Determine the time ratio of the chopper. (05 Marks)

OR

- Explain the effect of freewheeling diode with half wave controlled rectifier circuit and waveforms using inductive load. (10 Marks)
 - Explain the operation of step-up/down choppers with suitable circuit. Derive the relevant expression. (07 Marks)
 - A step-up chopper is used to deliver load voltage of 500V from a 220V dc source. If the blocking period of the thyristor is 80 μ s. Compute the required pulse-width. (03 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Explain the operation of the single phase half bridge inverter with RL load. Draw the relevant circuit and waveforms. (10 Marks)
- b. Explain the operation of the isolated forward converter with suitable circuit diagram and relevant waveforms. Mention the advantages and disadvantages. (10 Marks)

OR

- 6 a. Explain the types of errors in measurements. (07 Marks)
- b. Explain the operation of the multirange voltmeter with normal circuit and with multipliers connected in series string circuit. (07 Marks)
- c. A 1mA meter movement having an internal resistance of 100Ω is used to convert into a multirange ammeter having the range 0-10mA, 0-20mA, and 0-30mA. Determine the value of the shunt resistance required. (06 Marks)

Module-4

- 7 a. Explain the operation of dual slope integrating type DVM with basic principles and suitable block-diagram. (08 Marks)
- b. With suitable block diagram, explain the operation of measurement of time briefly. (07 Marks)
- c. A capacitance comparison bridge is used to measure a capacitive impedance at a frequency of 2kHz. This bridge constants at balance are $C_3 = 100\mu\text{F}$, $R_1 = 10\text{K}\Omega$, $R_2 = 50\text{K}\Omega$, $R_3 = 100\text{K}\Omega$. Find the equivalent series circuit of the unknown capacitance. (05 Marks)

OR

- 8 a. With suitable block diagram and table explain the operation of successive approximation DVM. (08 Marks)
- b. With suitable block diagram approach explain the operation of the digital frequency meter. (07 Marks)
- c. Find the equivalent parallel resistance and capacitance that causes a Wien bridge to null with the following component values $R_1 = 3.1\text{K}\Omega$, $C_1 = 5.2\mu\text{F}$, $R_2 = 25\text{K}\Omega$, $f = 2.5\text{kHz}$, $R_4 = 100\text{K}\Omega$. (05 Marks)

Module-5

- 9 a. Explain the operation of the resistive position transducer with construction and electrical equivalent circuit. (07 Marks)
- b. In the differential instrumentation amplifier using transducer bridge, $R_1 = 2.2\text{K}$, $R_F = 10\text{K}$, $R_A = R_B = R_C = 120\text{K}$, $E = +5\text{V}$ and op-amp supply voltage = $\pm 15\text{V}$, the transducer is a transistor with the following specifications. $R_T = 120\text{K}$ at a reference temperature of 25°C . Temperature coefficient of resistance = $-1\text{K}/^\circ\text{C}$. Determine the output voltage at 0°C and 100°C . (06 Marks)
- c. Explain the PLC structure with block diagram. And also explain the PLC operation with PLC operation diagram. (07 Marks)

OR

- 10 a. Explain the operation of the LVDT with construction, various core positions of it, and variation of output voltage vss displacement. (10 Marks)
- b. What is the significance of analog weight scale? Using strain gauge bridge circuit for analog weight scale explain its operation briefly. (05 Marks)
- c. With Bell circuit diagram, explain the operation of the Programmable Logic Controller (PLC) relays. (05 Marks)