

USN

--	--	--	--	--	--	--	--	--	--

06MAT31

**Third Semester B.E. Degree Examination, January 2013**  
**Engineering Mathematics – III**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. Obtain the fourier expansion of

$$f(x) = \begin{cases} -\pi, & -\pi < x < 0 \\ x, & 0 < x < \pi \end{cases} \quad \text{and hence } \sum \frac{1}{(2n-1)^2} = \frac{\pi^2}{8} \quad (07 \text{ Marks})$$

- b. Find the half range cosine series of

$$f(x) = \begin{cases} \frac{1}{4} - x, & \text{in } 0 < x < \frac{1}{2} \\ x - \frac{3}{4}, & \text{in } \frac{1}{2} < x < 1 \end{cases} \quad (06 \text{ Marks})$$

- c. Obtain the constant term, first coefficients of cosine and sine terms in the fourier series expansion of the function given by the following table:

x	0	1	2	3	4	5
y	9	18	24	28	26	20

(07 Marks)

- 2 a. Find the fourier transform of

$$f(x) = \begin{cases} 1 - |x|, & \text{for } |x| \leq 1 \\ 0, & \text{for } |x| > 1 \end{cases}$$

Hence deduce that  $\int_0^{\infty} \frac{\sin^2 t}{t^2} dt = \frac{\pi}{2}$  (07 Marks)

- b. Find  $f(x)$ , if  $\tau_s \{f(x)\} = \frac{s}{s^2 + 1}$ , (fourier sine transform). (07 Marks)

- c. Find finite fourier cosine transform of  $\left(1 - \frac{x}{\pi}\right)^2$  in  $0 < x < \pi$ . (06 Marks)

- 3 a. Find the partial differential equation representing all planes that are at a perpendicular distance 'p' from the origin. (07 Marks)

- b. Solve  $\frac{\partial^2 z}{\partial x \partial y} = \sin x \sin y$ , for which  $\frac{\partial z}{\partial y} = -2 \sin y$  when  $x = 0$  and  $z = 0$ , if  $y$  is an odd multiple of  $\pi/2$ . (07 Marks)

- c. Solve  $y^2 p - xyq = x(z - 2y)$  (06 Marks)

- 4 a. Derive arc dimensional wave equation. (07 Marks)

- b. Solve  $\frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} = 0$ , subject to the conditions  $u(0, y) = 0$ ,  $u(\pi, y) = 0$ ,  $u(x, \infty) = 0$  and  $u(x, 0) = k \sin 2x$  (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.



USN

--	--	--	--	--	--	--	--	--	--

06ES33

### Third Semester B.E. Degree Examination, January 2013

#### Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

#### PART – A

- 1 a. Design a minimum two level gate combinational network that detects the presence of six illegal code group (decimal 10 to 15) in a 4 bit that represent BCD code by providing a logic 0 and lighting a red LED. (08 Marks)
- b. Simplify the following expressions using Karnaugh map. Implement the simplified circuit using the gates as indicated.
  - i)  $f(w, x, y, z) = \sum m(1, 5, 7, 9, 10, 13, 15) + d(8, 11, 14)$  using NAND gates.
  - ii)  $f(A, B, C, D) = \pi m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$  using NOR gates. (12 Marks)
- 2 a. Simplify using Quine McCluskey minimization technique  
 $Y(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$  (12 Marks)
- b. Simplify the following Boolean function using variable entered map technique of taking z as the map entered variable:  
 $f(w, x, y, z) = \sum m(3, 5, 6, 7, 8, 9, 10) + dc(4, 11, 12, 14, 15)$  (08 Marks)
- 3 a. Design a 4 to 16 decoder using 2 to 4 decoders with active low enable and active low outputs. (08 Marks)
- b. Design a keypad interface to a digital system using ten line to four line encoder. (06 Marks)
- c. Design a binary full subtractor using basic gates. (06 Marks)
- 4 a. Implement the expression  $s = ad + b\bar{c} + bd$  using 4:1 mux. Choose b and d as select lines. (10 Marks)
- b. Design a combinational circuit that accepts two unsigned 2-bit binary number and provides 3 outputs.  
 Input : word A =  $A_1A_0$  word B =  $B_1B_0$   
 Output : A = B, A > B, A < B. (10 Marks)

#### PART – B

- 5 a. Explain the working of Master-Slave JK flip-flop with functional table and timing diagram. Show how race around condition is overcome. (08 Marks)
- b. Explain switch debouncing and its elimination using SR latch. (06 Marks)
- c. Obtain characteristic equations of JK and SR flip-flops. (06 Marks)
- 6 a. Explain the operation of Ring counter and twisted ring counter using shift register with the help of diagram. (08 Marks)
- b. Design a synchronous mod 6 counter using clocked JK flip-flop. (sequence 0, 2, 3, 6, 5, 1, 0) (12 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42-8 = 50, will be treated as malpractice.







- 3 a. Using superposition theorem find the voltage 'V' across  $3\Omega$  in Fig.Q.3(a). (09 Marks)  
 b. State and explain reciprocity theorem. (05 Marks)  
 c. State and prove Millman's theorem for current sources in series. (06 Marks)

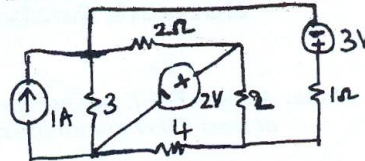


Fig.Q.3(a)

- 4 a. Applying Thevenin's theorem find current in  $2L$  in Fig.Q.4(a). (06 Marks)  
 b. Find  $I_L$  in Fig.Q.4(b) using Norton's theorem. (07 Marks)  
 c. What is the value of  $R_L$  for maximum power transfer in Fig.Q.4(c)? Also find the maximum power. (07 Marks)

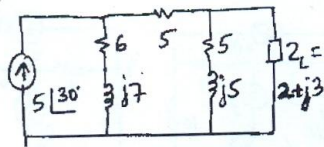


Fig.Q.4(a)

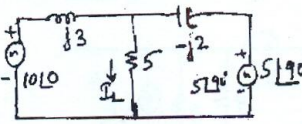


Fig.Q.4(b)

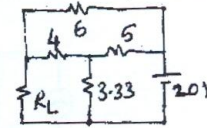


Fig.Q.4(c)

PART - B

- 5 a. A series RLC circuit has a bandwidth of  $600\text{Hz}$  and quality factor of 10. If the value of  $L$  is  $0.05\text{H}$ , find the value of  $C$ . (04 Marks)  
 b. For a two branch RL-RC parallel resonant circuit, determine the expression for resonant frequency. In this circuit for  $L = 0.4\text{H}$  and  $C = 40\mu\text{F}$ , obtain resonant frequency for the following values of  $R_L$  and  $R_C$  i)  $R_L = R_C = 80\Omega$ ; ii)  $R_L = 100$  and  $R_C = 80$ . (08 Marks)  
 c. Find band width of the antiresonant circuit shown in Fig.Q.5(c), with following conditions  
 i)  $Q$  of the inductive branch = 100; ii) Frequency of unity power factor =  $1\text{MHz}$ ;  
 iii)  $L = 100\mu\text{H}$  and iv) Internal resistance of generator  $R_g = 10\Omega$ . (08 Marks)

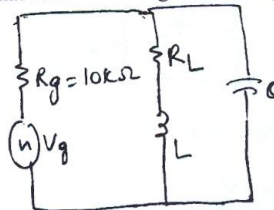


Fig.Q.5(c)

- 6 a. In the network shown in Fig.Q.6(a), the switch  $K$  is changed from position 1 to position 2 at  $t = 0$ , steady - state being established at position 1. Find :  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0+$ . (08 Marks)

- b. The switch K is closed at  $t = 0$  in Fig.Q.6(b). At  $t = 0^-$  all capacitor voltages and inductor currents are zero. Three node to datum voltages are identified as  $V_1, V_2$  and  $V_3$ . Find  $V_1, V_2, V_3, \frac{dv_1}{dt}, \frac{dv_2}{dt}, \frac{dv_3}{dt}$  and  $\frac{d^2v_3}{dt^2}$  at  $t = 0^+$ . (12 Marks)

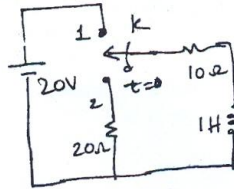


Fig.Q.6(a)

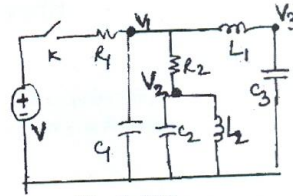


Fig.Q.6(b)

- 7 a. Find the Laplace transform of  $x(t)$  shown in Fig.Q.7(a). (06 Marks)  
 b. In Fig.Q.7(b), switch K is opened at  $t = 0$ , steady-state reached at  $t = 0^-$ . Using Laplace transform, find  $I_L(s)$  and hence  $i_L(t)$ . Also find the value of  $i_L(t)$  at  $t = 0.5$  seconds. (10 Marks)  
 c. Find the initial and final values of  $f(t)$  when  $F(s) = \frac{9s+10}{S(s+2)}$ . (04 Marks)

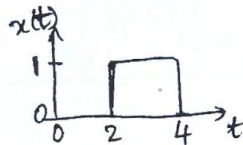


Fig.Q.7(a)

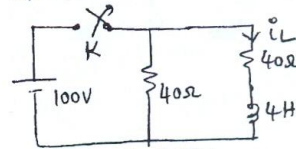


Fig.Q.7(b)

- 8 a. Compute  $V_1$  and  $V_2$  in Fig.Q.8(a) with admittance matrix  $[Y] = \begin{bmatrix} 0.3 & -0.1 \\ -0.1 & 0.15 \end{bmatrix}$ . (08 Marks)  
 b. Obtain the open-circuit impedance parameters for the network shown in Fig.Q.8(b). (08 Marks)  
 c. Obtain T-parameters in terms of z-parameters. (04 Marks)

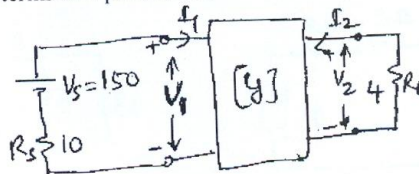


Fig.Q.8(a)

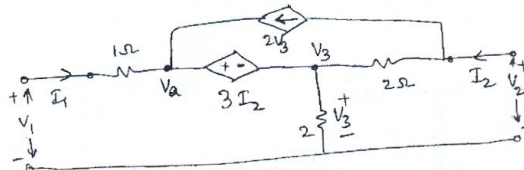


Fig.Q.8(b)

\*\*\*\*\*







**PART – B**

- 5 a. With the help of a neat block diagram, explain the working of a pulse generator. (08 Marks)  
 b. Draw a block diagram of frequency synthesizer, showing the waveforms at various points. Explain carefully how the synthesizer operates. (08 Marks)  
 c. Draw the block diagram of a function generator and explain the method of producing sine waves. (04 Marks)
- 6 a. An unbalanced Wheatstone bridge is given in Fig.Q6(a). Calculate the current through the galvanometer. (05 Marks)

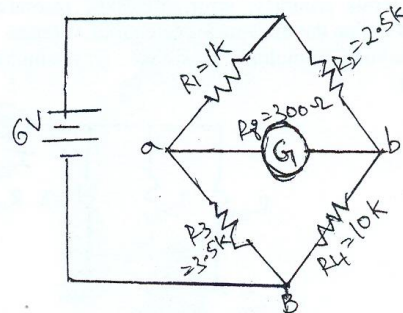


Fig.Q6(a)

- b. Describe the operation of a Kelvin's bridge. (06 Marks)  
 c. A capacitance comparison bridge (similar angle bridge) is used to measure a capacitive impedance at a frequency of 2 kHz. The bridge constants at balance are  $C_3 = 100 \mu\text{f}$ ,  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 50\text{k}\Omega$ ,  $R_3 = 100\text{k}\Omega$ . Find the equivalent series circuit of the unknown impedance. (03 Marks)  
 d. Explain the operation of Weins bridge along with the derivation for frequency. (06 Marks)
- 7 a. What is a resistive position transducer? Explain its construction with a diagram. (04 Marks)  
 b. An AC LVDT has following data. Input = 6.3V, output = 5.2V, range  $\pm 0.5$  in. Determine,  
 i) the output voltage vs core position for a core movement going from +0.45 in to -0.30 in.  
 ii) The output voltage, when the core is -0.25 in. from the centre. (03 Marks)  
 c. Explain the construction and operation of LVDT. (10 Marks)  
 d. Mention the advantages of electrical transducers. (03 Marks)
- 8 a. List various types of temperature transducers & describe the applications of each. (05 Marks)  
 b. Explain in detail about LCD, with diagrams. (10 Marks)  
 c. Explain AC signal conditioning system with general schematic diagram. (05 Marks)

\*\*\*\*\*

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

06ES36

**Third Semester B.E. Degree Examination, January 2013**  
**Field Theory**

Time: 3 hrs.

Max. Marks:100

**Note:** Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. Define the following : i) Coulomb's law    ii) Electric field intensity    iii) Gauss law. (06 Marks)  
 b. State the prove divergence theorem. (06 Marks)  
 c. Let  $\vec{D} = 5r^2 \mathbf{a}_r \text{ mc / mt}^2$  for  $r < 0.08\text{mt}$   
 and  $\vec{D} = \frac{0.1}{r^2} \mathbf{a}_r \text{ mc/mt}^2$  for  $r > 0.08 \text{ mt}$ . Find  $\rho_v$  for i)  $r = 0.06 \text{ mt}$     ii)  $r = 0.1 \text{ mt}$ . (08 Marks)
- 2 a. An electric potential is given by  $V = \frac{60 \sin \theta}{r^2}$ . Find  $v$  and  $\vec{E}$  at  $(3, 60^\circ, 25^\circ)$ . (08 Marks)  
 b. Derive the integral and point form of continuity equation. (06 Marks)  
 c. Derive the boundary conditions for perfect dielectric materials of permittivities  $\epsilon_1$  and  $\epsilon_2$ . (06 Marks)
- 3 a. Obtain Poisson's and Laplace's equations from Maxwell's first equation. (06 Marks)  
 b. Verify that the potential field given below satisfy Laplace's equation. (06 Marks)  
 $V = 2x^2 - 3y^2 + z^2$ .  
 c. Derive the expression for capacitance of a co - axial cable using Laplace's equation. (08 Marks)
- 4 a. State and explain Biot - Savart law. Using this, find the magnetic flux density at the centre of a circular loop of radius 'a' mt. (08 Marks)  
 b. Magnetic field intensity in free space is  $\vec{H} = 10\rho^2 \mathbf{a}_\phi \text{ A/mt}$ . Determine i)  $\vec{J}$     ii) Integrate over the circular surface  $\rho = 1\text{mt}$  all  $\phi$  and  $Z = 0$ . (06 Marks)  
 c. Explain scalar and vector magnetic potentials. (06 Marks)

PART - B

- 5 a. Derive the equation for magnetic force between two differential current elements. (06 Marks)  
 b. Given the ferrite material which is to be operating in a linear mode with  $\vec{B} = 0.05\text{T}$  and  $\mu_R = 50$ . Calculate the values for  $\chi_m$ ,  $\vec{M}$  and  $\vec{H}$ . (06 Marks)  
 c. Define self inductance. Find the same of a Solenoid with air core has 200 turns and a length of 60cm core with radius 3cm. Derive the formula used. (08 Marks)
- 6 a. Derive the Maxwell's equation in point form as derived from Faraday's law. (06 Marks)  
 b. Determine the frequency at which conduction current density and displacement current density are equal in a medium with  $\sigma = 2 \times 10^{-4} \text{ S/mt}$  and  $\epsilon_r = 81$ . (06 Marks)  
 c. List the Maxwell's equation in differential and integral form as applied to time - varying fields. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 7 a. Discuss the uniform plane wave propagation in a good conducting medium. (06 Marks)  
b. A 9375 MHz uniform plane wave is propagating in polystyrene ( $\mu_r = 1$ ,  $\epsilon_r = 2.56$ ). If the amplitude of electric field intensity is 20V/m and the material is assumed to be lossless. Find i) Phase constant ii) Wavelength iii) Velocity of propagation iv) Intrinsic impedance v) Magnetic field intensity. (10 Marks)  
c. State and explain Poynting theorem. (04 Marks)
- 8 a. Define Standing wave ratio (SWR). Find the value of SWR when reflection co-efficient ( $\Gamma$ ) =  $\pm \frac{1}{2}$ . (04 Marks)  
b. Derive the expressions for transmission co-efficient and reflection co-efficient. (08 Marks)  
c. Determine the reflection co-efficient and transmission co-efficient for a wave traveling in air and incident on a dielectric medium with  $\mu = \mu_0$  and  $\epsilon_r = 4$ . Also find out average incident, reflected and transmitted powers. Show that average power is conserved. (08 Marks)

\*\*\*\*\*