

USN

--	--	--	--	--	--	--	--	--	--

MATDIP301

Third Semester B.E. Degree Examination, December 2012

Advanced Mathematics – I

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions.

- 1** a. Find the modulus and amplitude of the complex number $1 - \cos \alpha + i \sin \alpha$. (05 Marks)
 b. If z_1 and z_2 are two complex numbers, show that $|z_1 + z_2|^2 + |z_1 - z_2|^2 = 2\{|z_1|^2 + |z_2|^2\}$. (05 Marks)
 c. Find the fourth roots of $-1 + i\sqrt{3}$. (05 Marks)
 d. If $2 \cos \theta = x + \frac{1}{x}$, prove that $2 \cos r\theta = x^r + \frac{1}{x^r}$. (05 Marks)
- 2** a. Find the n^{th} derivative of $e^{2x} \cos^3 x$. (07 Marks)
 b. Find the n^{th} derivative of $\frac{x}{x^2 - 5x + 6}$. (06 Marks)
 c. If $y = e^{a \sin^{-1} x}$, prove that $(1 - x^2)y_{n+2} - (2n + 1)xy_{n+1} - (n^2 + a^2)y_n = 0$. (07 Marks)
- 3** a. Find the angle between the pair of curves $r = 6 \cos \theta$, $r = 2(1 + \cos \theta)$. (07 Marks)
 b. Find the pedal equation of the curve $r^2 = a^2 \sin 2\theta$. (06 Marks)
 c. Obtain the Maclaurin's series expansion of the function $\sqrt{1 + \sin 2x}$. (07 Marks)
- 4** a. If $u = x^2y + y^2z + z^2x$, prove that $\frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} = (x + y + z)^2$. (05 Marks)
 b. If $u = \tan^{-1}\left(\frac{x^3y^3}{x^3 + y^3}\right)$, prove that $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \frac{3}{2} \sin 2u$. (05 Marks)
 c. If $u = x + y + z$, $v = y + z$, $z = uvw$, find Jacobian of x, y, z with respect to u, v, w . (05 Marks)
 d. If $z = f(x, y)$ and $x = e^u + e^v$ and $y = e^{-u} - e^v$, prove that $\frac{\partial z}{\partial u} - \frac{\partial z}{\partial v} = x \frac{\partial z}{\partial x} - y \frac{\partial z}{\partial y}$. (05 Marks)
- 5** a. Obtain the reduction formula for $\int_0^{\pi/2} \cos^n x \, dx$ and hence evaluate $\int_0^{\pi/2} \cos^6 x \, dx$ and $\int_0^{\pi/2} \cos^9 x \, dx$. (07 Marks)
 b. Evaluate $\int_0^1 \int_{x^2}^{\sqrt{x}} xy(x + y) \, dy \, dx$. (06 Marks)
 c. Evaluate $\int_0^a \int_0^x \int_0^{x+y} e^{x+y+z} \, dz \, dy \, dx$. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8=50, will be treated as malpractice.

- 6 a. Define Gamma and Beta functions. Show that $\beta(m, n) = 2 \int_0^{\pi/2} \sin^{2m-1} \theta \cos^{2n-1} \theta d\theta$. (07 Marks)
- b. Prove that $\int_0^{\infty} x^2 e^{-x^4} dx \times \int_0^{\infty} e^{-x^4} dx = \frac{\pi}{8\sqrt{2}}$. (07 Marks)
- c. Evaluate $\int_0^1 (\log x)^6 dx$. (06 Marks)
- 7 a. Solve the equation $\frac{dy}{dx} + x \tan(y-x) = 1$. (06 Marks)
- b. Solve $x^2 y dx - (x^3 + y^3) dy = 0$. (07 Marks)
- c. Solve $(e^y + y \cos xy) dx + (x e^y + x \cos xy) dy = 0$. (07 Marks)
- 8 a. Solve the equation $(D^3 + 1)y = 0$, where $D = \frac{d}{dx}$. (06 Marks)
- b. Solve the equation $(D^2 - 2D + 1)y = x e^x$. (07 Marks)
- c. Solve $\frac{d^2 y}{dx^2} + 2 \frac{dy}{dx} + y = e^{2x} - \cos^2 x$. (07 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10MAT31

Third Semester B.E. Degree Examination, December 2012
Engineering Mathematics – III

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Find the Fourier series of $f(x) = x - x^2$, $-\pi \leq x \leq \pi$. Hence deduce that

$$\frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots = \frac{\pi^2}{12} \quad (07 \text{ Marks})$$

Is the above deduced series convergent? (Answer in Yes or No)

- b. Define : i) Half range Fourier sine series of $f(x)$
ii) Complex form of Fourier series of $f(x)$

Find the half range cosine series of $f(x) = x$ in $0 < x < 2$. (07 Marks)

- c. Obtain a_0 , a_1 , b_1 in the Fourier expansion of y , using harmonic analysis for the data given.

x	0	1	2	3	4	5
y	9	18	24	28	26	20

(06 Marks)

- 2 a. Find the Fourier transform of

$$f(x) = 1 - x^2 \quad \text{for } |x| \leq 1$$

$$= 0 \quad \text{for } |x| > 1$$

Hence evaluate $\int_0^{\infty} \frac{x \cos x - \sin x}{x^3} \cos\left(\frac{x}{2}\right) dx$ (07 Marks)

- b. Find the Fourier sine transform of $\frac{e^{-ax}}{x}$ (07 Marks)

- c. Find the Fourier cosine transform of
- $$f(x) = 4x, \quad \text{for } 0 < x < 1$$
- $$= 4 - x, \quad \text{for } 1 < x < 4$$
- $$= 0, \quad \text{for } x > 4$$

(06 Marks)

- 3 a. i) Write down the two dimensional heat flow equation (p d e) in steady state (or two dimensional) Laplace's equation. Just mention.
ii) Solve one dimensional heat equation by the method of separation of variables. (07 Marks)
- b. Using D'Alembert's method, solve one dimensional wave equation. (07 Marks)
- c. A string is stretched and fastened to two points l apart. Motion is started by displacing the string in the form of $y = a \sin(\pi x/l)$ from which it is released at time $t = 0$. Show that the displacement of any point at a distance x from one end at time t is,

$$y(x, t) = a \sin\left(\frac{\pi x}{l}\right) \cos\left(\frac{\pi c t}{l}\right)$$

Start the answer assuming the solution to be

$$y = (C_1 \cos(px) + C_2 \sin(px))(C_3 \cos(cpt) + C_4 \sin(cpt)) \quad (06 \text{ Marks})$$

- 4 a. Fit a linear law, $P = mW + C$, using the data

P	12	15	21	25
W	50	70	100	120

(06 Marks)

- b. Find the best values of a and b by fitting the law $V = at^b$ using method of least squares for the data,

V (ft/min)	350	400	500	600
t (min)	61	26	7	26

Use base 10 for algorithm for computation.

(07 Marks)

- c. Using simplex method,

$$\text{Maximize } Z = 5x_1 + 3x_2$$

$$\text{Subject to, } x_1 + x_2 \leq 2 ; 5x_1 + 2x_2 \leq 10 ; 3x_1 + 8x_2 \leq 12 ; x_1, x_2 \geq 0.$$

(07 Marks)

PART - B

- 5 a. Use Newton-Raphson method, to find the real root of the equation $3x = (\cos x) + 1$. Take $x_0 = 0.6$. Perform two iterations.

(06 Marks)

- b. Apply Gauss-Seidel iteration method to solve equations

$$20x + y - 2z = 17$$

$$3x + 20y - z = -18$$

$$2x - 3z + 20z = 25$$

Assume initial approximation to be $x = y = z = 0$. Perform three iterations.

(07 Marks)

- c. Using Rayleigh's power method to find the largest eigen value and the corresponding eigen vector of the matrix.

$$A = \begin{bmatrix} 6 & -2 & 2 \\ -2 & 3 & -1 \\ 2 & -1 & 3 \end{bmatrix}$$

Take $[1 \ 0 \ 0]^T$ as the initial approximation. Perform four iterations.

(07 Marks)

- 6 a. Use appropriate interpolating formula to compute $y(82)$ and $y(98)$ for the data

x	80	85	90	95	100
y	5026	5674	6362	7088	7854

(07 Marks)

- b. i) For the points (x_0, y_0) (x_1, y_1) (x_2, y_2) mention Lagrange's interpolation formula.

- ii) If $f(1) = 4$, $f(3) = 32$, $f(4) = 55$, $f(6) = 119$; find interpolating polynomial by Newton's divided difference formula.

(07 Marks)

- c. Evaluate $\int_0^6 \frac{1}{1+x^2} dx$, using

- i) Simpson's $1/3^{\text{rd}}$ rule ii) Simpson's $3/8^{\text{th}}$ rule iii) Weddle's rule, using

x	0	1	2	3	4	5	6
$f(x) = \frac{1}{1+x^2}$	1	0.5	0.2	0.4	0.0588	0.0385	0.027

(06 Marks)

- 7 a. Solve the wave equation $\frac{\partial^2 u}{\partial t^2} = 4 \frac{\partial^2 u}{\partial x^2}$ subject to $u(0, t), u(4, t) = 0$, $u_t(x, 0) = 0$ and $u(x, 0) = x(4 - x)$ by taking $h = 1$, $k = 0.5$ upto four steps. (07 Marks)
- b. Solve two dimensional Laplace equation at the pivotal or nodal points of the mesh shown in Fig.Q7(b). To find the initial values assume $u_4 = 0$. Perform three iterations including computation of initial values. (07 Marks)

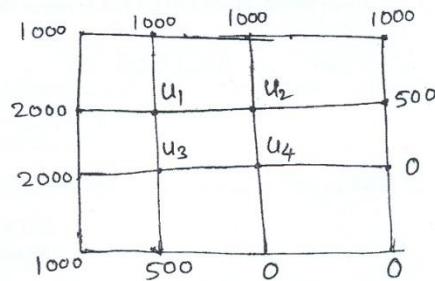


Fig.Q7(b)

- c. Solve the equation $\frac{\partial u}{\partial t} = \frac{\partial^2 u}{\partial x^2}$, subject to the conditions $u(x, 0) = \sin \pi x$, $0 \leq x \leq 1$; $u(0, t) = u(1, t) = 0$. Carry out computations for two levels, taking $h = 1/3$, $k = 1/36$. (06 Marks)
- 8 a. Find the z-transform of $\frac{n}{3^n} + 2^n n^2 + 4 \cos(n\theta) + 4^n + 8$ (07 Marks)
- b. State and prove i) Initial value theorem ii) Final value theorem of z-transforms. (07 Marks)
- c. Using the z-transform solve $u_{n+2} + 4u_{n+1} + 3u_n = 3^n$ with $u_0 = 0, u_1 = 1$. (06 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10ES32

Third Semester B.E. Degree Examination, December 2012
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain reverse recovery time of a semiconductor diode. (07 Marks)
 b. Explain avalanche breakdown and zener breakdown. (06 Marks)
 c. For the diode circuit shown in Fig.Q.1(c), calculate I_D , V_D and V_R , assume $V_r = 0.7V$. (07 Marks)

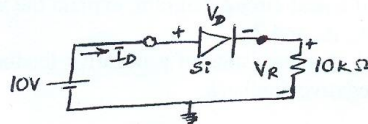


Fig.Q.1(c)

- 2 a. Explain with a neat diagram, fixed bias configuration to fix the operating point. (06 Marks)
 b. Derive the expression for stability factors for fixed-bias circuit, with respect to I_{CO} , V_{BE} and β . (06 Marks)
 c. For the emitter bias circuit shown in Fig.Q.2(c), find the values of R_C , R_E and R_B using the following specifications $I_{C(sat)} = 10 \text{ mA}$, $I_{CQ} = 1/2 I_{C(sat)}$, $V_C = 20V$. Assume silicon transistor with $\beta = 100$. (08 Marks)

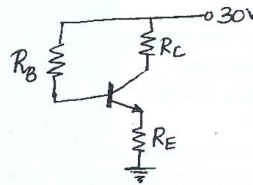


Fig.Q.2(c)

- 3 a. Obtain the expressions for voltage gain Z_{in} and Z_o of common-base configuration using AC equivalent circuit with r_e model. (07 Marks)
 b. Explain with a neat circuit diagram, Emitter follower configuration justify how. Voltage gain is approximated to unity. (07 Marks)
 c. For the circuit shown in Fig.Q.3(c) determine V_{CC} if $A_v = -160$ and $r_o = 100 \text{ k}\Omega$, take $\beta = 100$. (06 Marks)

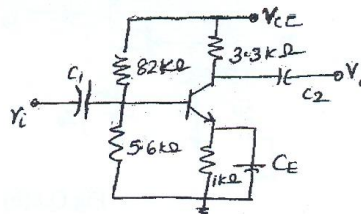


Fig.Q.3(c)

- 4 a. Describe the factors that affect the low frequency response of a BJT-CE amplifier. (10 Marks)
 b. For the common-base amplifier shown in Fig.Q.4(b) calculate r_e , R_i , A_v , C_s , C_c , over all lower cut-off frequency $\beta = 75$ and $r_0 = \infty$. (10 Marks)

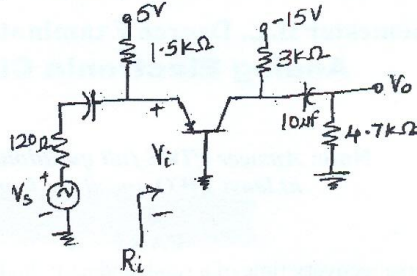


Fig.Q.4(b)

PART - B

- 5 a. With the help of a neat circuit diagram, explain the working of a Dalington Emitter-Follower and derive Z_i , A_i , A_v and Z_o . (10 Marks)
 b. List the general characteristics of a negative feedback amplifier and derive the expression for gain with negative feedback. (10 Marks)
- 6 a. Explain the operation of a class B push-pull power amplifier with the help of a neat circuit diagram and also draw the i/p and o/p waveforms of the class B power amplifier, justify elimination of even harmonic distortion. (10 Marks)
 b. A class B push-pull amplifier operating with $V_{CC} = 25V$ provides a 22V peak signal to an 8Ω load. Find. Peak load current, dc current drawn from the supply, input power, output power, circuit efficiency, power dissipation. (10 Marks)
- 7 a. Derive the expression for frequency of a Wein Bridge oscillator and explain the operation using a neat circuit diagram. (08 Marks)
 b. In a transistor Colpitts oscillator $C_1 = 1nF$ and $C_2 = 1000nF$. Find the value of L for a frequency of 100 kHz. (06 Marks)
 c. A crystal has the following parameter $L = 0.3344$, $C_M = 1pF$, $C = 0.065 pF$ and $R = 5.5 K\Omega$. Calculate the series resonant frequency, parallel resonant frequency and find the Q of the crystal. (06 Marks)
- 8 a. Explain the operation of JFET amplifier using fixed bias configuration. Draw the JFET small signal model and derive expressions for input impedances output impedance and voltage gain A_v . (10 Marks)
 b. For the JFET amplifier shown in Fig.Q.8(b). Calculate Z_i , Z_o and A_v . (10 Marks)

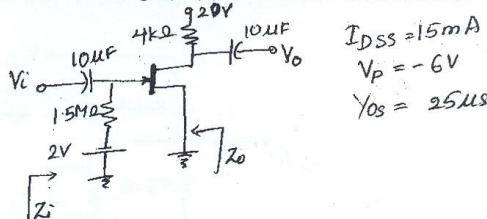


Fig.Q.8(b)

USN

--	--	--	--	--	--	--	--	--	--

06ES32

Third Semester B.E. Degree Examination, January 2013
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain the diode equivalent circuit with its characteristics. (06 Marks)
- b. Explain transition and diffusion capacitance in an P-N junction diode. (06 Marks)
- c. Plot the transfer characteristic for the circuit shown in Fig. Q1(c) and write the transfer characteristic equation. Sketch V_o if $V_i = 40\sin\omega t$. Assume $V_K = 1$ V for the diode. (08 Marks)

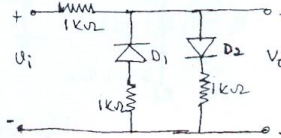


Fig. Q1 (c)

- 2 a. Define operating point. Explain its significance. (04 Marks)
- b. Derive an expression for I_B , I_C and V_{CE} for an collector feedback bias. (08 Marks)
- c. Design an emitter stabilized network shown in Fig. Q2(c) using the following data: (08 Marks)

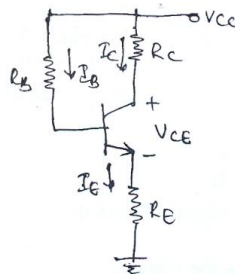


Fig. Q2 (c)

$$I_{CQ} = \frac{1}{2} I_{C(sat)}, V_{CEQ} = \frac{1}{2} V_{CC}$$

$$V_{CC} = 20 \text{ V}, I_{C(sat)} = 10 \text{ mA}$$

$$\beta = 120, R_C = 4R_E$$

Assume $I_E \cong I_C$

- 3 a. Derive an expression for Z_i , Z_o , A_v and A_i for common-emitter configuration using emitter bias with unbypassed R_E . (Using r_e model) (10 Marks)
- b. For the fixed bias configuration shown in Fig. Q3(b), calculate
 - i) A_{VNL} , Z_i and Z_o
 - ii) A_v , A_{VS} and A_i
 - iii) Calculate V_o , if $V_S = 20$ mV. Take $\beta = 100$ (10 Marks)

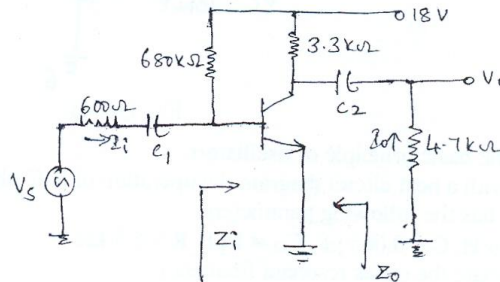


Fig. Q3 (b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 4 a. Derive an expression for Miller input capacitance and Miller output capacitance. (10 Marks)
 b. For the circuit shown in Fig. Q4(b), calculate the following:
 i) r_e , ii) Input resistance R_i iii) Mid band voltage gains $A_V = \frac{V_o}{V_s}$ and $A_{V_S} = \frac{V_o}{V_s}$
 iv) lower cutoff frequency due to C_C . For transistor $\beta = 100$ and $r_o = \infty$. (10 Marks)

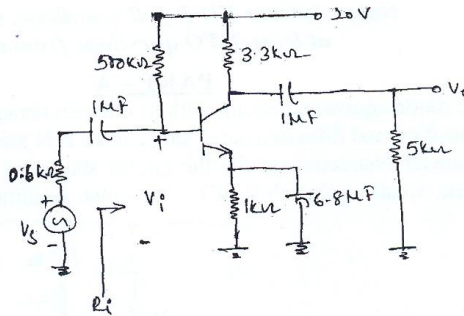


Fig. Q4 (b)

PART - B

- 5 a. Explain the difference between cascade and cascode connections and its application. (05 Marks)
 b. Derive an expression for Z_i , Z_o , A_v for Darlington emitter follower. (10 Marks)
 c. Explain feed back amplifier topologies. (05 Marks)
- 6 a. With a neat circuit diagram, explain transformer coupled class A amplifier and derive the expression for AC power delivered to the load, show maximum efficiency is 50%. (10 Marks)
 b. The following readings are available for a power amplifier. Calculate the second harmonic distortion in each case:
 i) $V_{CEQ} = 10\text{ V}$, $V_{CE(max)} = 18\text{ V}$, $V_{CE(min)} = 1\text{ V}$ (05 Marks)
 ii) $V_{CEQ} = 10\text{ V}$, $V_{CE(max)} = 19\text{ V}$, $V_{CE(min)} = 1\text{ V}$ (05 Marks)
 c. For the circuit shown in Fig. Q6 (c) the input signal results in a peak base current of 1 mA
 i) Calculate the ac output power.
 ii) Calculate the dc input power dissipated by the circuit.
 iii) Calculate the efficiency. (05 Marks)

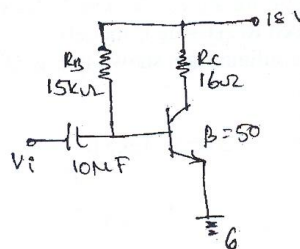


Fig. Q6 (c)

- 7 a. Explain the basic principle of oscillators. (06 Marks)
 b. Explain with a neat circuit diagram the operation of R-C phase shift oscillator. (08 Marks)
 c. A crystal has the following parameters:
 $L = 0.334\text{ H}$, $C = 0.065\text{ pF}$, $C_M = 1\text{ pF}$, $R = 5.5\text{ k}\Omega$
 i) Calculate the series resonant frequency.
 ii) Calculate the parallel resonant frequency.
 iii) Find the Q of the crystal. (06 Marks)

- 8 a. Derive an expression for A_v , Z_i and Z_o for an JFET source follower. (10 Marks)
- b. For the network shown in Fig. Q8 (b), $V_{GSQ} = -2.86$ V, $I_{DQ} = 4.56$ mA, $I_{DSS} = 16$ mA, $V_P = -4$ V, $Y_{OS} = 30$ μ s. Determine i) g_m ii) r_d iii) z_i and iv) z_o without r_d and v) A_v without r_d . (10 Marks)

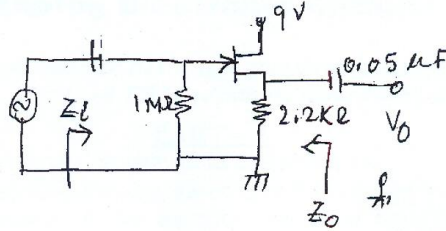


Fig. Q8 (b)

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, December 2012

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Define canonical Minterm form and canonical Maxterm form. (05 Marks)
 b. Design a three-input, one output minimal two-level gate combinational circuit which has an output equal to 1 when majority of its inputs are at logic 1 and has an output equal to 0 when majority of its inputs are at logic 0. (05 Marks)
 c. Minimize the following multiple output functions using K-MAP:
 $f_1 = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 4, 5, 14, 15)$
 $f_2 = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$ (10 Marks)
- 2 a. Use a K-Map to simplify that following functions:
 i) $f(A, B, C, D) = (A + B + \bar{C})(\bar{B} + \bar{D})(\bar{A} + C)(B + C)$
 ii) $f(A, B, C, D) = \pi(1, 2, 4, 5, 7, 8, 10, 11, 13, 14)$ (10 Marks)
 b. Find all the prime implicants of the function
 $f(a, b, c, d) = \sum(7, 9, 12, 13, 14, 15) + \sum d(4, 11)$
 Using Quine Mc Clusky algorithm. (10 Marks)
- 3 a. Reduce the given function using MEV technique:
 i) $f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + ABCE + ABC\bar{E} + d(\bar{A}\bar{B}CD + \bar{A}\bar{B}CE)$
 ii) $f = m_0 + m_1F + m_2 + m_4F + m_6(E + \bar{E}) + m_7F + m_{10}E$
 $+ m_{12} + m_{15}F + d(m_3F + m_9\bar{F} + m_{11}\bar{E} + m_8E)$ (10 Marks)
 b. Write the condensed truth table for a 4 to 2 line priority encoder with a valid output where the highest priority is given to the highest bit position or input with highest index and obtain the minimal sum expressions for the outputs. (06 Marks)
 c. Describe general working principle of decoder. (04 Marks)
- 4 a. Explain the working principle of four-bit parallel fast look ahead carry adder. (10 Marks)
 b. Design a comparator to check if two n-bit numbers are equal. Configure this using cascaded stages of 1-bit comparators. (10 Marks)

PART - B

- 5 a. With a neat diagram, explain the working of Master-Slave JK flip-flop along with waveforms. (10 Marks)
 b. Explain switch debouncer using SR latch with waveforms. (10 Marks)
- 6 a. Explain universal shift register with the help of logic diagram, mode control table. (10 Marks)
 b. Design and implement a divide-by-10 asynchronous counter using T FFS. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8=50, will be treated as malpractice.

- 7 a. Design and implement a synchronous BCD counter using J-K FFS. (10 Marks)
 b. A sequential circuit has one input and one output state diagram is as shown in Fig.Q7(b). Design the sequential circuit with J-K flip-flop.

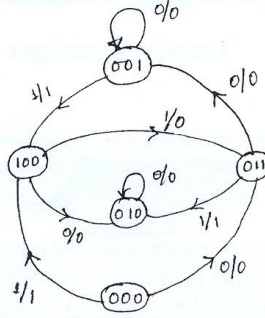


Fig.Q7(b)

(10 Marks)

- 8 a. Design a sequence detector for the following sequence 1, 0, 1, 1, 1 with overlap. Write the state diagram and logic diagram. (10 Marks)
 b. A sequential circuit has two flip-flops A and B, two inputs x and y, and an output z. The flip-flop input functions and the circuit output functions are as follows:

$$J_A = xB + \bar{y}\bar{B}; \quad K_A = x\bar{y}\bar{B}$$

$$J_B = x\bar{A}; \quad K_B = x\bar{y} + A$$

$$z = xyA + \bar{x}\bar{y}\bar{B}$$

Obtain the logic diagram, state table and state equations, also state diagram. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--	--	--

10ES34

Third Semester B.E. Degree Examination, December 2012

Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Define and distinguish the following network elements:
 - i) Linear and non-linear
 - ii) Active and passive
 - iii) Lumped and distributed
 - iv) Ideal and practical current sources

(08 Marks)
- b. Write the mesh equation for the circuit shown in Fig.Q1(b) and determine mesh currents using mesh account analysis. (06 Marks)

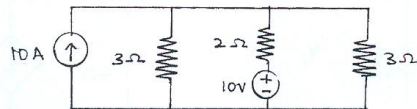


Fig.Q1(b)

- c. Reduce the network shown in Fig.Q1(c) to a single voltage source in series with a resistance using source shift and source transformations. (06 Marks)

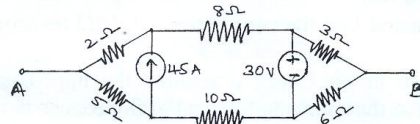


Fig.Q1(c)

- 2 a. Define the following terms with reference to network topology. Give examples.
 - i) Tree
 - ii) Graph
 - iii) Sub-graph
 - iv) Tie-set
 - v) Cut-set

(10 Marks)
- b. Construct a tree for the network shown in Fig.Q2(b) so that all loop currents pass through 7Ω. Write the corresponding the set matrix. (06 Marks)

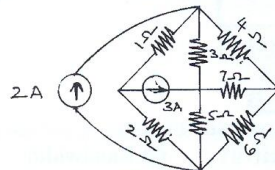


Fig.Q2(b)

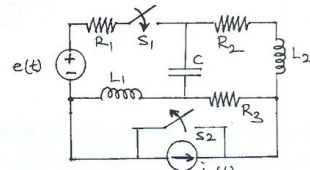


Fig.Q2(c)

- c. What are dual networks? Draw the dual of the circuit shown in Fig.Q2(c). (04 Marks)

- 3 a. Using superposition theorem, obtain the response I for the network shown in Fig.Q3(a).

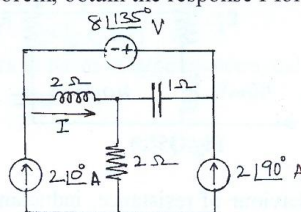


Fig.Q3(a)

(08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 3 b. Verify reciprocity theorem for the circuit shown in Fig.Q3(b). (06 Marks)

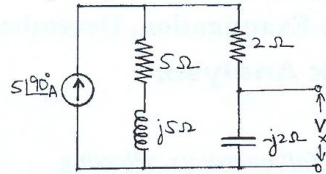


Fig.Q3(b)

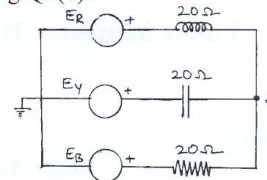


Fig.Q3(c)

- c. Use Millman's theorem to determine the voltage V_S of the network shown in Fig.Q3(c), given that $E_R = 230 \angle 0^\circ$ V ; $E_Y = 230 \angle -120^\circ$ V and $E_B = 230 \angle 120^\circ$ V. (06 Marks)

- 4 a. For the network shown in Fig.Q4(a), obtain the Thevenin's equivalent as seen from the terminals p and q. (08 Marks)

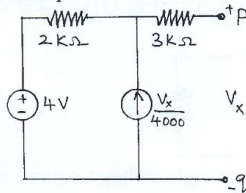


Fig.Q4(a)

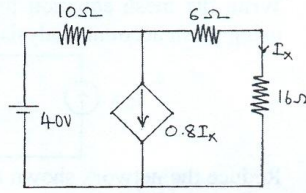


Fig.Q4(b)

- b. State Norton's theorem and find the current through 16Ω resistor using Norton's theorem in Fig.Q4(b). (06 Marks)
- c. For the network shown in Fig.Q4(c), determine the impedance Z_X such that maximum power is transferred from the source to the load of impedance Z_X .

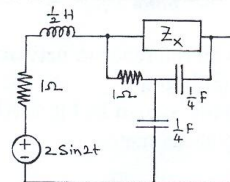


Fig.Q4(c)

(06 Marks)

PART - B

- 5 a. Define the following terms with reference to resonant circuit:
 i) Resonance ii) Q-factor iii) Selectivity iv) Bandwidth (06 Marks)
- b. A series RLC circuit has $R = 10\Omega$, $L = 0.01\text{H}$ and $C = 0.01\mu\text{F}$ and it is connected across 10 mV supply. Calculate: i) f_0 ; ii) Q_0 ; iii) Bandwidth ; iv) f_1 and f_2 ; v) I_0 (10 Marks)
- c. Determine R_L and R_C for which the circuit shown in Fig.Q5(c) resonates at all frequencies.

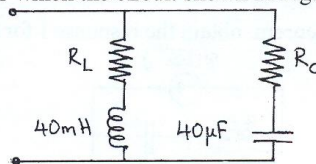


Fig.Q5(c)

(04 Marks)

- 6 a. Explain the transient behaviour of resistance, inductance and capacitance. Also explain the procedure for evaluating transient behaviour. (10 Marks)

- 6 b. In the network shown in Fig.Q6(b), 'K' is changed from position 'a' to 'b' at $t = 0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$, if $R = 1000 \Omega$, $L = 1H$ and $C = 0.1\mu F$ and $V = 100V$. Assume that the capacitor is initially uncharged. (10 Marks)

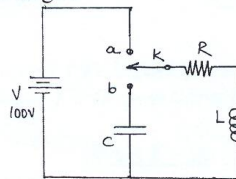


Fig.Q6(b)

- 7 a. Assuming that the staircase waveform of Fig.Q7(a) is not repeated, find its Laplace transform. If this voltage wave is applied to a RL series circuit with $R = 1\Omega$ and $L = 1H$, find the current $i(t)$. (10 Marks)

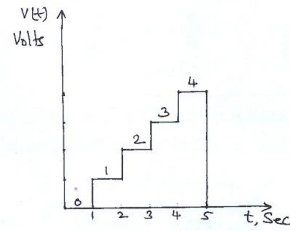


Fig.Q7(a)

- b. The network shown in Fig.Q7(b) was in steady state before $t = 0$. The switch is opened at $t = 0$. Find $i(t)$ for $t > 0$, using Laplace transform. (10 Marks)

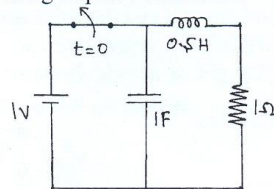


Fig.Q7(b)

- 8 a. Obtain the h-parameters for the network shown in Fig.Q8(a). (10 Marks)

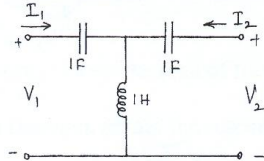


Fig.Q8(a)

- b. Obtain ABCD parameters in terms of z-parameters and hence show that $AD - BC = 1$. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10IT35

Third Semester B.E. Degree Examination, January 2013
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Discuss briefly the different types of static errors of a measuring instrument. (06 Marks)
- b. Calculate the value of the multiplier resistance on the 100 V range of a dc voltmeter that uses a 100 mA meter movement with an internal resistance of 100 Ω . (06 Marks)
- c. Explain the principle and operation of a true rms responding voltmeter with the help of a suitable block diagram. (08 Marks)
- 2 a. List the advantages of digital instruments over analog instruments. (04 Marks)
- b. Explain with the help of a neat diagram the working of a digital frequency meter. (07 Marks)
- c. A $3\frac{1}{2}$ digit voltmeter is used for measuring voltage,
 - i) Find the resolution of the instrument. (04 Marks)
 - ii) How would be a reading 15.53 be displayed on 100 V range? (05 Marks)
- d. Discuss briefly the general specifications of a digital voltmeter.
- 3 a. Draw the basic block diagram of an oscilloscope and explain the functions of each block. (08 Marks)
- b. Explain the functions of various controls on the front panel of a CRO. (04 Marks)
- c. Write an explanatory note on dual beam CRO with a block diagram. (08 Marks)
- 4 a. Explain the operation of a sampling oscilloscope with a block diagram. Mention the advantage of a sampling oscilloscope. (10 Marks)
- b. Discuss the operation of a digital storage oscilloscope with a neat block diagram. (10 Marks)

PART – B

- 5 a. Explain the operation of a sweep frequency generator with the help of a suitable block diagram. Mention its applications. (08 Marks)
- b. What is a frequency synthesizer? Explain the operation with a suitable block diagram. (08 Marks)
- c. Write a brief note on function generator. (04 Marks)
- 6 a. With the help of a neat circuit diagram, explain the operation of the wien bridge. Derive the expression for the frequency. Mention the limitations of this bridge. (08 Marks)
- b. What is meant by 'Wagner's earth connection'? Explain with a suitable diagram. (06 Marks)
- c. A highly sensitive galvanometer can detect a current as low as 0.1 μ A. This galvanometer is used in the wheatstone bridge as a detector. The resistance of the galvanometer is negligible. Each arm of the bridge has a resistance of 1 K Ω . The input voltage applied to the bridge is 20 V. Calculate approximately the smallest change in resistance which can be detected. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 7 a. List the factors to be considered while selecting a transducer for a given application. (04 Marks)
- b. Explain the method of measuring displacement using LVDT with a suitable diagram. State the advantage and disadvantages of LVDT. (10 Marks)
- c. A 100Ω strain gage with a gage factor of 1 is affixed to a metal bar. The bar is stretched and this causes a change in resistance of 0.001Ω . Find the change in length if the original length is 10 cm. (06 Marks)
- 8 a. Describe the operation of a piezo electric transducer with a diagram. Mention its disadvantage. (06 Marks)
- b. What are the advantages of LCD displays over LED displays? (04 Marks)
- c. Explain the procedure of measuring power using a bolometer in a bridge circuit. Mention the range of power which can be measured in this method. (06 Marks)
- d. Write an explanatory note on signal conditioning. (04 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10ES36

Third Semester B.E. Degree Examination, January 2013
Field Theory

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

1.
 - a. Define 'Electric field intensity'. Derive an expression for electric field intensity' (\vec{E}) at a point due to many charges. (07 Marks)
 - b. Point charges of 50 nC each are located at A(1, 0, 0) B(-1, 0, 0) C(0, 10) and D(0, -1, 0)m, find the total force on the charge at A and also find \vec{E} at A. (05 Marks)
 - c. Given $\vec{D} = 5\vec{r}$ C/m², prove divergence theorem for a shell region enclosed by spherical surfaces at $r = a$ and $r = b$ ($b > a$) and centred at the origin. (08 Marks)
2.
 - a. Find the electric field intensity at point x(1, 2, -1) given the potential $V = 3x^2y + 2y^2z + 3xyz$. (05 Marks)
 - b. Derive boundary conditions between conductor and free space if different ' ϵ '. (08 Marks)
 - c. Show that capacitance of co-axial cable is $C = \frac{2\pi \epsilon L}{\ln[b/a]}$ F with usual notations. (07 Marks)
3.
 - a. With usual representations derive Poisson's equation. (05 Marks)
 - b. Verify that the potential field given below satisfies the Laplace's equation $V = 2x^2 - 3y^2 + z^2$. (05 Marks)
 - c. A large spherical cloud of radius 'b' has a uniform volume charge distribution of ρ_v C/m³, find the potential distribution and electric field intensity at any point in space using Laplace. (10 Marks)
4.
 - a. State and explain Biot – Savart law. (06 Marks)
 - b. Calculate the value of vector current density in cylindrical co –ordinates at p(1.5, 90°, 0.5) if $\vec{H} = \frac{2}{\rho} \cos 0.2\phi \vec{a}_\phi$. (06 Marks)
 - c. Given $\vec{H} = 20r^2 \vec{a}_\phi$ A/m, determine the current density J also determine the total current that crosses the surface $r = 1$ m, $0 < \phi < 2\pi$ and $z = 0$ in cylindrical co-ordinate. (08 Marks)

PART – B

5.
 - a. Derive Lorentz force equation. (05 Marks)
 - b. Find the force per meter length between two long parallel wires separated by 10 cm in air and carrying a current of 10A in the same direction. (05 Marks)
 - c. Calculate the inductance of a solenoid of 200 turns wound tightly on a cylindrical tube of 6 cm diameter. The length of the tube is 60 cm, the solenoid is in air. Derive the equation for 'L'. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 6 a. Explain Maxwell's equations for time varying fields. (10 Marks)
 b. Find amplitude of displacement current density (J_D) in the free space within a large power distribution transformer $\vec{H} = 10^6 \cos(377t + 1.2566 \times 10^6 z) \vec{a}_y$ A/m. (05 Marks)
 c. Given $H = H_m e^{j(\omega t + \beta z)} \vec{a}_x$ A/m in free space find \vec{E} . (05 Marks)
- 7 a. Starting from Maxwell's equations obtain the general wave equations in electric and magnetic field. (10 Marks)
 b. A 300 MHz uniform plane wave propagates through fresh water for which $\sigma = 0$, $\mu_r = 1$, $\epsilon_r = 78$, calculate :
 i) Attenuation constant
 ii) Phase constant
 iii) Wave length
 iv) Intrinsic impedance. (05 Marks)
 c. State and explain Poynting theorem. (05 Marks)
- 8 a. Define transmission co-efficient and reflection co-efficient deduce the relationship between them. (06 Marks)
 b. A traveling \vec{E} field in the free space of amplitude 100 v/m strikes a perfect dielectric as shown in Fig. Q8(b). Determine E_t . (10 Marks)

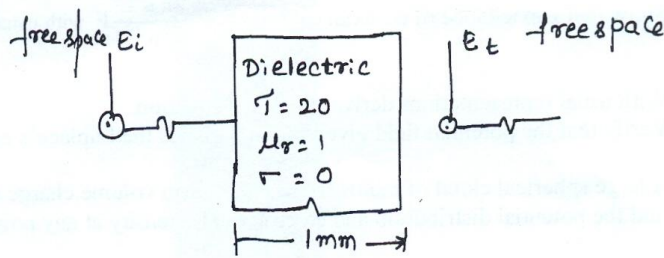


Fig. Q8(b)

- c. Write a note on SWR. (04 Marks)
